RESTRICTED

TM 11-235

WAR DEPARTMENT

TECHNICAL MANUAL

(A)

RADIO SETS SCR-536-A, SCR-536-B

SCR 536-D SCR-536-E May 14, 1943

STK-NO-6DI3137

Note.—This is not a revision. This manual contains only C 1, 15 December 1943, to the 14 May 1943 edition placed at the back following the original text, and will not be issued to individuals possessing that edition.

RESTRICTED

TECHNICAL MANUAL)

WAR DEPARTMENT. WASHINGTON, May 14, 1943.

No. 11-235 RADIO SETS SCR-536-A, SCR-536-B, AND SCR-536-C

DESTRUCTION NOTICE

Depending upon the time and materials available, when the capture of this equipment by the enemy is certain, completely destroy it by one or more of the following means:

1. Explosives such as grenades or TNT. 2. Incendiaries such as wood, oil, and gasoline.

3. Axes, hammers, large rocks, or other hard, heavy objects

such as hand generators, dynamotors, etc.

Removal of the chassis from the case will simplify the above means of destruction. When this is done he sure to smash crystals and holders, tubes, coils, microphone, earphone, and hatteries:

Destroy all instruction books, Technical Manuals, circuit diagrams, or other literature for this radio set at the same time.

SAFETY NOTICE

The voltages used in this radio set are not high enough to be injurious. A slight shock, of negligible magnitude, may result by touching the antenna and case at the same time, when the set is transmitting.

	Pr	regraphs
SECTION I.	Description	1-9
	Employment	
III.	Functioning of parts	24-38
		39-78
V.	Supplementary data	
INDEX		Page 82

*This manual supersedes TM 11-235, March, 1942.

SIGNAL CORPS

Section I

DESCRIPTION

Paragra
Use
Components, weights, and dimensions
Total weights
Source of power and power requirements.
Distance range
Frequency coverage
Modes of transmission and reception.
Contrels
Description of components.

Use.—Radio set SCR-536-(*) is designed for short-range two-way voice conversation. Descriptively, it is a press-to-talk portable radio telephone, receiving and transmitting on the same frequency. No skill is required to operate it.

a. The set is self-contained; all equipment necessary for reception and transmission is contained in one aluminum case.

b. The set may be held in either hand when operating, although it is designed and bladneed for left-hand operation. The microphone and earphone are attached to the case in such manner that the set resembles a hand telephone. An adjustable carrying strap is attached to the case. (See fig. 1 and 2.)

"Badlo sets SCI-030-A, SCI-030-B, and SCI-030-C are allike, for all practical purposes. The different suffic letters indicate different procurements. For eventual control of the sufficient sufficient sufficient procurements. For eventual varieties and sufficience exists between types. Similarly the component parts, radio receivers and transmitters BC-031-A, BC-031

2. COMPONENTS, WEIGHTS, AND DIMENSIONS.


Quan.	Article	Dimensions (Inches) ¹					
tity		Height	Width	Depth	Length	Diam- eter	Unit weight (pounds)
1 2 2 1	Battery BA-37 (1.5 volts) Battery BA-38 (103.5 volts) Preliminary instructions Radio receiver and transmit-	61/6 113/4 11 151/4	11362 836 336	11362		1%4	0, 55 1, 10
	ter BC-611-(*) (with coils, crystals and tubes, but without batteries).						
1	Set of crystals (spare).2 Tube set GK-174 (spare):				- 1		
	Consisting of: 1 tube VT-171						
	1 tube VT-172						. 0
	1 tube VT-173						. 0:
1	2 tube VT-174_ Box BX-49 Containing:						. 0:
1	12 sets of crystals (trans- mitting and receiving)						
	12 sets of antenna coils. 12 sets of r-f tank coils.						
	(1 set of coils and crystal for each of 12 operat- ing frequencies),						

Component of SCR-536-A only. Component of SCR-536-C only.

- Total weights.—Total weight of radio set SCR-536-(*), including batteries, is 5.5 pounds. Over-all dimensions and weights of components are given in paragraph 2.
- Source of power and power requirements.—Radio receiver and transmitter BC-611-(*) is battery powered. Space for both A and B batteries is provided in the housing. (See fig. 1.)
- and B batteries is provided in the housing. (See fig. 1.)

 a. The filament or A battery BA-37, rated at 1.5 volts, is cylindrical
 in shape and fits into the round compartment in the housing.
- b. The B battery BA-38, rated at 103.5 volts, is oblong in shape and fits into the oblong compartment in the housing. (The bottom of the case has a hinged cover which permits access to the batteries and radio chassis.)
- c. Power requirements.—Batteries should last 15 hours, under almost continuous operation.

Battery	Drain receiving	Deals transmitting	
A battery BA-37 1.5 volts	0.25 amperes	0.30 amperes.	7
B battery BA-38 103.5 volts	11 milliamperes	35 milliamperes.	

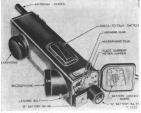

PISCRE 1.—Radio set SCE-536-(*)—showing battery compartment.

- 5. Distance range.—The set is designed to operate over distances from 100 feet to I mile. The dependability of operation at the greater distance will depend on the terrain and the freedom from signal absorbing optics such as steed buildings, trees, bills, and telephone and power lines between the two sets. This is particularly there for sets operating at the higher frequencies in the band. The maximum range may be considerably greater when operating over water or in the air.
- 6. Frequency coverage.—Badio set SGR-305-(*) is crystal controlled no both reception and transmission, and will operate over the frequency range of 2500 to 6000 kilocycles. However, each unit is can be made to operate at any frequency in the hand by proper choice of crystals and coils. For correct performance, each set must be adjusted to the crystals used. The coils and crystal changes and their adjustments cannot be made by the operator, but are repair points. (See sec. IV.) withstreams we as substreams.

- Modes of transmission and reception.—Radio set SCR-536-(*) transmits and receives amplitude modulated voice signals only.
- Controls.—a. Send-receive.—A press-to-talk switch, conveniently located under the finger tips when the radio set is held in normal operating position, is the only control required for operation of this equipment. (See fig. 1.)
- b. On-off.—By fully extending the telescopic antenna rod, the set is automatically turned on. When the telescopic antenna rod is fully retracted the set is automatically turned off. (The bottom section of the antenna operates the on-off power switch.)
- c. Volume.—No volume control is used with this set. The volume in the earphone is set to a normal level by the design of the equipment.
 - d. Tuning.—The operator is not required to make tuning adjustments of any kind. (See par. 6.)
 - 9. Description of components—a. The housing which incloses radio receiver and transmitter Be-Gall-(*) is an alumium casting. Its interior is divided into three compartments, one for the radio classic, one for the A latter, BA-S7, and one for the B hattery BA-S8. Two projections from the housing contain the earphone lands that the projections are so spead and of such length that we must. These projections are so spead and of such length that we must. These projections are so spead and of such length that we must. The projections are so spead in the projection for talking the project position for talking the projection for talking the project position for talking talking the project position for talking the project position for talking the project position for talking talking the project position for talking t
- b. The press-to-talk switch, mounted on the side of the case, operates the change-over switch on the radio chassis. This converts the set from a receiver to a transmitter. This switch is so located that it may be operated easily with the fingertips when the set is held in the left hand.
- c. The bottom cover hinges to the housing and is provided with a slot into which a latching bolt fits. It is through this end of the housing that the chassis and batteries are inserted or removed. A contact terminal board inside the bottom cover provides the connections between the batteries and the radio chassis.
- d. A small eard holder below the press-to-talk switch contains a plastic eard on which the operating frequency and date of battery replacement are marked. This card is protected from wear by a transparent cover. To remove the eard from its container the bottom cover must be opened. (See fig. 1).
- c. The top cover of the set contains an opening for the antenna rod. This cover is held in place by a mounting screw which holds

the chassis securely in the housing. Spring battery contacts and a spacer for the A battery BA-37, fastened to the top cover, make electrical connections to the batteries.

f. An antenna cap, attached to the top cover on the outside by a chain, protects the telescopic rod antenna against weather conditions when the set is not in use.

Note.—Early issues of radio set SCR-539-A were furnished with a crystal microphose and crystal earphone. All later issues of SCR-509-A and radio sets SCR-509-B and SCR-509-C and SCR-509-B and industry components are electrically and mechanically interchangeable with the crystal units they replace.

SECTION II EMPLOYMENT

Paragr	ar
Initial procedure	1
Installation	1
Preparation for use	1
Starting the set	3
Receiving	1
Transmitting	1
Turning off set. Operation over long periods.	3
Operation over long periods	3
Netting	3
Change of frequency	1
Power output	2
Replacing batteries	:
Operation in the rain	5
Poor reception and transmission	2

10. Initial procedure.—Unpack the equipment carefully to prevent damage or loss of components. Check against list of components in paragraph 2. Also note the channel on which the radio receiver and transmitter are alined.

receiver and transmitter are alined.

11. Installation,—a General.—The set is furnished by the manufacturer with everything contained in the housing except the batteries. To put the set into operation, the batteries must be inserted in their proper place.

b. Installation of batteries BA-37 and BA-38—Open the radio set bottom cover by turning the latching bolt knurled nut in a counterclockwise direction, until the nut begins to turn with difficulty. Then press the cover against the case and push the bolt away from the housing. Release the cover and it will open. (See fig. 1.)

(1) Battery BA-37 (filament or A battery) is cylindrical in shape and fits into the round compartment of the radio set housing. Insert the battery into the housing with its positive end out. The positive terminal is marked with a large positive (+) sign. It can be identified also by a small raised metal button. The raised button permits positive identification when installing battery in darkness. (2) Battery BA-38 (B battery) is oblong in shape and fits into

(a) Date() passes (b) lattery) is obtoing in snape and its into the oblong compartment of the radio set housing. It also must be placed into the battery compartment with the positive (+') end out. The positive terminal is marked with a large plus (+) sign and also can be identified by the small raised metal batton.

Norm-Before dosting the radio set bottom cover, mark the date of battery installation on the data card beared in the potest part below the press-to-talk switch. The card is removed by sliding it out of the bottom of the pocket. The transparent protective cover will come out with the card. Ense the old date that is marked on the card, and put on the new one. When replacing the card, ensemble to put the transparent protective cover will card.

(3) After the batteries are installed close the battom cover of the unido set by pressing the cover against the housing with one hand, while the other hand moves the latching bold into the cover slot and tightests the knurreled nut by turning it clockwise. The cover then should be pressed against a soild object and the knurreled nut tightened by hand until it turns with great difficulty. This will assure positive contact between batteries and battery contacts.
12. Preparation for use.—Before railor receiver and transmitter

BC-611-(*) can be placed in operation, the following must be done: a. Uncrew the antenna cap which covers the telescopic antenna. (See fig. 1.) To prevent losing it, this cap is attached to the housing by a small chain. Serew the cap on the threaded metal stud on top of the housing. This will prevent the cap from rattling against the housing when operating the set. See that the chain is not warned around the antenna roul and that there is no charge of it is

touching the rod.

b. Pull the antenna out gently until all four sections of the rod are fully extended. The antenna then will be about 39 inches long.

c. The unit is now held in the left hand, in the same manner as a telephone handset, and is ready for use as a radiotelphone set.

(See fig. 2)

13. Starting the set.—In succeeding paragraphs radio set SCR-139. Clay will be referred to as "the set." The set is turned on when the antenna is fully extended. This is accomplished by a small lever attached to the antenna red which operates the power switch on the radio chassis. A rawhing noise in the earphone will indicate that the receiver is on. Also a click will be heard when the switch number sanae over

Caution .- A stop at the lower end of the antenna rod prevents it from being pulled out of the case, but the bottom section of the antenna must be fully extended since it operates the power switch on the chassis BY WHICH THE SET IS TURNED ON.



14. Receiving.—The set is normally in the receive position so that the operator can hear signals from another set if it is transmitting on the same frequency. The set should be held in the hand as shown in figure 2. The antenna will then extend above the head in an approximately vertical position. This is important for best reception and transmission.

15. Transmitting .- a. In order to transmit, the press-to-talk switch on the side of the housing must be depressed. This is done with the fingers of the hand holding the unit. The operator then can speak to the operator of the other set. The press-to-talk switch makes the necessary circuit changes to convert the receiver into a

transmitter.

b. In order to receive, the press-to-talk switch must be released when transmission is completed.

c. When the operator is speaking into the microphome, the speech level should be varied according to distance of transmission. It should be very soft for short distances. The operator should speak clerity, and should take care that the press-to-tak witch is declarity, and should take care that the press-to-tak witch is decompletion of conversation. In the beginning and end of his speech. There is natural tendency to look the switch down when through speaking, and to forget to press the switch before starting to speak. A little for a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after pressing the very little growth or a moment after the pressing the very little growth or a moment after the pressing the very little growth or a moment after the pressing the very little growth or a moment after the pressing the very little growth or a moment after the pressing the very little growth or a moment after the pressing the very little growth or a moment after the pressing the very little growth or a moment after the pressing the very little growth or a moment after the pressing the very little growth or a moment after the press and the pressing the very little growth or a moment after the press and the pressing the very little growth or a moment after the pressing the very little growth or a moment after the pressing the very little growth or a moment after the press t

16. Turning off set.—Telescope the antenna into the case. The bottom section of the antenna rod must be pushed into the case as far as it will go. This will turn off the set. The operator can ear the toggle switch snap over. Put the antenna cap in place, covering the antenna when the set is not in use.

17. Operation over long periods.—When operating the st for long periods, it will be found less tring to carry the st bung over the shoulder rather than to carry it in the hand. To carry it in the name, tengthen the strap by pulling the strap side toward the manner, lengthen the strap by pulling the strap side toward the plot arm between the strap and the set housing the strap side to the strap side of the strap side of the strap side of the set of the strap side of the side o

18. Netting—For two-way conversation, two sets adjusted to operate on the same frequency are required. Two sets operating at different frequencies will be unable to converse with each other. More than two operators can engage in conversation by the use of more set operating on the same frequency. Because of the receiver arrangement used, it is possible to operate several receiver without rearrangement used, it is possible to operate several receiver without the contract of the contract

- 19. Change of frequency.—Changing the operating frequency of the unit requires a change of the two crystals and of two coils. Coil and crystal equipment is available to cover the frequency range of 33 megacycles to 6 megacycles if required. Special equipment is required for retuning of the sets, and a trained technican must do the job. The frequency presetting and realimement procedure will be found in section I/V of this book.
- 20. Power output.—Maximum power output is obtained in the transmitting position with the antenna fully extended. If the units are not at a great distance from each other and a reduction of the power radiated is desired, telescope one or two of the top sections of the antenna. The bottom section must remain fully extending the processing the proce
- 21. Replacing batteries.—See procedure given in paragraph 11a.
 Replace both batteries even though one is in better condition than the
 other. This will reduce the chances of battery trouble.
- Note.—When sets are to be placed in storage for long periods of time, remove the batteries from the case. This will prevent the batteries from becoming wedged in the battery compartment, should they swell when aging.
- 22. Operation in the rain.—The set is designed to exclude water, but, if operated in the rain, it may be found that the water film covering the antenna insulator at the base of the antenna acts as a short circuit between the antenna and case, making the set weak or inoperative. Wipe the insulator frequently with a dry cloth to improve operation.
- 23. Poor reception and transmission .- a. If the distance between sets in communication with each other is between 100 feet and 1 mile, and the transmission is poor, it may be that the batteries are weak. The batteries are designed to give about 15 hours of use, assuming that the unit is on for long periods of time and that the operator is transmitting much of the time. They will last much longer if not used constantly. A sign of weak batteries is a low noise level in the earphone when the set is in the receive position and no other station is being received. Another cause of poor reception may be signal absorbing objects, such as steel buildings, trees, hills, power and telephone lines, and large metal objects between the two units. The straight-line distance between units should be as clear of such objects as possible. Operation often will be improved by moving one or both sets to new locations. Placing the set as high as possible, as on top of a hill or building, will help to increase the range of operation. Be sure that the antenna is fully extended, held, as nearly as possible, in a vertical position, and clear of obstructions for several feet around it. When operating the unit in the underbrush, keep the antenna

Precautions should be taken particularly in the early morning when dew is on the ground, or after a rainfall. Conditions of this kind may render the unit inoperative.

may render the unit moperative.

b. If the set does not work when the antenna is extended, that is,
no sound is heard in the earphone, check to see that the bottom section
of the antenna is catended out of the case to its full length. This is
necessary to operate the power switch on the chassis.

 If the set still does not work, refer to section IV for further corrective measures.

SECTION III

Paraless described	ragraj
Receiver Tunetioning	:
Receiver functioning Basic receiver circuit	1
R·f amplifier	1
Converter-oscillator	- 1
Rf amplifier Converter-oseillator I-f amplifier.	. 2
Second detector—first a-f amplifier	- 4
Second a-f amplifier	0
Transmitter functioning	- 3
Basic transmittes elecuit	- 3
Oscillator	3
B.f. execution and the contract of the contrac	3
R-f power amplifier	3
Microphone amplifier Modulator	3
- Modulator	3
Description of parts	3

Note:—This description is based on radio set SCR-595-C. SCR-598-A and B are similar except for minor differences.

24. Receiver functioning.—In the receive position, the set acts as a five-tube superheterolyne receiver consisting of one r-f amplifier stage, using a tube VT-174, one cocillator-mixer stage using a tube VT-177, one choice detector and first audio amplifier stage using a two VT-178, one choice detector and first audio amplifier stage using a tube VT-178, and one audio power output stage using a tube VT-174. The functional diagram of receiver is shown in figure 3.

25. Basic receiver circuit;—c. The antenna is series tuned by the mica trimmer C., The signal voltage developed across C, is amplified by tube V₁ and applied to the grid of tube V₂. In V₃, the mixer-occillator tube, the incoming signal is mixed with the oscillator signal generated in the tube and produces a best frequency signal of 450 Ke. The oscillator uses a crystal in a Piezec circuit, and functions at 455 ke above the carrier or incoming signal frequency. The receiver.

crystal M., therefore is 455 kc higher in frequency than the transmitter

b. The beat frequency or i-f signal produced in the mixer is amplified by tube Va and is applied to the diode section of tube Va. Due to the detection process, the modulated i-f signal is demodulated, and an audio voltage is impressed across R20, the grid resistor of the pentode section of tube V4. The signal is then applied to the grid of tube V., the power amplifier, where it is further amplified and then applied to the earphone.

26. R-f amplifier .- a. Capacitor C. is not necessary for the receiving function, but serves to block the d-c component of the plate voltage from the antenna rod in the transmit position. The inductance L. is a loading coil which aids in resonating the antenna. Resistor R., the grid resistor of V., provides a d-c path for the bias applied to the grid of tube V, and a high impedance to the r-f current, preventing it getting into the avc circuits. Capacitor C, is the antenna tuning capacitor. Capacitor C. is an r-f bypass for the filament circuit to reduce regeneration. Capacitor C2 bypasses the r-f current from the screen. Resistor R., helps make the bypassing of C. more effective as it increases the impedance of the path through the B battery BA-38. This arrangement is commonly called a decoupling filter, Resistor R., also reduces the screen current.


b. The permeability-tuned inductance L2 provides the r-f plate load for tube V1 and is resonated by a capacitance made up of the distributed capacitance of the coil, the output capacitance of tube V., the input capacitance of the tube V., and the capacitance of circuit wiring. L, is adjusted to its operating frequency by a movable pow-

dered iron slug.

c. Capacitor C, and resistor R., make up a decoupling filter for the plate circuit of tube V1. The resistor R10 also serves to lower the plate voltage of tube V, which reduces its plate current and gives more

economical operation of the B battery BA-38.

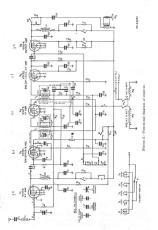27. Converter-oscillator .- a. Capacitor C10 is the coupling capacitor which provides passage for the r-f current to the grid of tube V., but prevents the d-c at the plate of tube V. from reaching the grid. Resistor R, is the grid resistor of tube V. Resistors R, and R, make up the grid leak which provides the bias voltage for the oscillator grid as well as the bias voltage for the audio output tube VT-174. A voltage suitable for biasing purposes is produced across these resistors because of the d-c component of the grid current which exists as a result of driving the oscillator grid positive. The three resistors R25, R7, and R5 make up a voltage divider to provide the proper values of bias for tubes V1, V2, and V2 when necessary to reduce regeneration.



b. Capacitors C₁₁ and C₁₁, and resistors R₂ and R₃, make up a filter for the stunnatic volume control (ave) voltage applied to the grids returned to the stunnatic volume control (ave) voltage is obtained from the director lead resistance made up of resistors R₃ and R₄. The filter morrows the audion component of the grid voltage (a), and R₄. The filter morrows the substance component of the grid voltage (a), and C₁₁, C₁₂, C₁₂, C₁₃, C₁₃, C₁₄, C₁

c. Capacitor C₄ is a neutralizing capacitor. It reduces the voltage of the oscillator frequency on the signal grid due to coupling within the tube, by feeding back a voltage of the oscillator frequency out

of phase with the internally coupled voltage.

d. The r-f choke L₁ is a shunt feed arrangement for the screen grid of tube V_r. It provides a low-resistance d-c path and a high-impedance r-f path to the screen grid.
e. The crystal M, connected between the No. 1 grid (oscillator grid).

and the screen grid provides the coupling necessary for oscillation. This arrangement is known as the Pierce oscillator circuit.

f. Capacitor C₁₁ and resistor R₁, make up a decoupling filter for the screen circuit of tube V₂.

28. 1.4 amplifate.—The first 1-ξ transformer T, (two windings) is wound on iron cores and is surrounded by an iron sheeve to increase the inductance of the primary and secondary coids and to reduce their size. The coid is are tuned by the trimmers C₁ and C₁. Resistor R_c, which is contained within the shield, serves to breaden the response of the transformer. Capactic C₁, and recistor R_c makes up a decoupling filter for the pattern of the transformer. Capactic C₁ and first forth E are the complicit of the V₂. Capactic C₃ in the V₄ is comprise a decoupling filter for the plate circuit of the V₄.

29. Second detector—first a-f amplifier.—a. The second i-f transformer T_o is also wound on an iron core and is surrounded by an

iron sleeve. The trimmer C, tunes the secondary.

iron sieeve. The trimmer C₁₅ times the secondary.
b. Resistor R₁, is the detector load across which the audio voltage is obtained. Resister R₁₅ and capacitors C₂₅ and C₂₁ make up a filter to remove the i-f component from the audio component of the detector voltage.

c. Capacitor C₂₂ couples the detector to the grid of the 1st audio amplifier, and prevents the d-c component of the detector output from biasing this grid.

d. Resistor R₂₀ is the grid resistor of the pentode section of tube V₄. As it has 10 million ohms of resistance, the small amount of grid current which exists in the tube and flows through the resistor provides additional bias for this tuke on large signal inputs. Capacitor C_{p_1} is an i-f bypass to eliminate any i-f current which exists in the plate circuit from getting into the audio plate load resistor R_{12} . C_{12} bapcior C_{p_1} and resistor R_{13} . C_{13} bapcior C_{p_2} and resistor R_{13} the exceen. Register R_{p_1} is the plate load of tube V_{q_1} and C_{27} is the coupling capacitor.

30. Second a-f amplifier.—a. Resistor R₂₁ is the grid resistor of tube V₅. Capacitor C₂₉ and resistors R₂₄ and R₁₆ make up a decoupling filter, for the screen of tube V₅. Resistor R₁₆ also helps

reduce battery drain by lowering the screen current.

b. The audio choke La provides a low resistance de- path for the plate current, and offers a high impedance path to the audio plate current. Capacitor C₂₀ and resistor R₁, make up a plate decoupling filter. Resistor R₁, also serves as a dropping resistor to lower the plate voltage. Capacitor C₂₀ prevents the d-c at the plate from reaching the earphone.


c. Notice that only one filament section of each of the tubes VT-174 is used in the receive position. This arrangement reduces the A

battery BA-37 drain.

31. Transmitter functioning.—In the transmit position only four tubes are used. The circuit consists of a crystal controlled oscillator in a Pierce circuit, which drives a tube VT-174 as an r-f power amplified. The r-f power amplifier is plate modulated by a modulating amplifier made up of a voltage amplifier stage and a modulator stage. The functional diagram of the transmitter is shown in fig. stage. The functional diagram of the transmitter is shown in fig.

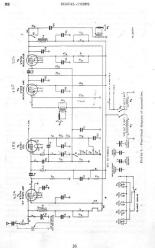32. Basic transmitter circuit,-a. The r-f carrier is generated in

- the oscillator section of tuke V_s. The crystal used for the transmitter is 455 ke lower in frequency than that used for the receiver. The generated r-f voltage is applied to the grid of tuke V_s where it is amplified and fed into the antenna. The antenna is coupled to the amplifier tank or tuned circuit by an impedance matching network of the v type in which the capacity between the antenna rod and housing makes up one shunt branch as
- b. The microphone output is amplified by the pentode section of the V_a and then applied to the grid of tube V, where it is further amplified. The output of tube V_i is then fed into the plate circuit of the V_i, it explains the value V_i is then fed into the plate circuit of the V_i, it explains the screen of tube VI is tied to the lower end of coil L_o the modulating voltage is introduced into the accreance circuit as well as the plate circuit.
- c. The earphone is also connected across the audio output so that the operator can hear what he is saying. This is known as sidetone.



33. Oscillator.—a. In the transmit position only the oscillator section of the tube VT-171 is utilized. Resistors R₁ and R₁ make up the grid leak which provides the bias voltage for the oscillator grid. The d-c component of the voltage developed across R₄ is used also for

the grid bias for the modulator tube V_s .

b. The rf choke L₀ provides a shunt feed arrangement for the screen grid. Capacitor C₁ determines the amount of feedback to the grid. Capacitor C₁₁ is the screen circuit bypass. Capacitors C₁₁, C₁₂, and C₂₁ are not necessary to the transmitter circuit; they are hold-overs from the receiver function. The same is true of resistors R₁, R₁₂, R₂, R₃, R₃, R₄, and R₅. These resistors, however, do tie the N₀ 3 arried of tube V to cround.

34. R-f power amplifier.—a. Capacitor C_s is the coupling capacitor and provides a path for the r-f current to the grid of tube V_s but prevents the d-c at the screen of tube V_s from being applied to the grid. Resistor R_s is the grid leak and provides the bias voltage for the grid of tube V_s. Capacitor C_s is the r-f bypass for the screen grid.

b. Coal L₂ is the ref amplifier tank coil and C₂ is the rf amplifier tank turning capacitor. Capacitor C₂, also exts as on branch of the network connecting the antenna to the amplifier tank. The capacity between the antenna rod and the bonsing acts as the other shunt branch of the *n etwork. In the receive position this autenna capacitane the agrant of the turing apacitanes of the attenna. The antenna bonness a part of the turing apacitanes of the attenna. The antenna bonding indicatance.
c. Canacitor, C.; the black circuit ref brances. The current insket in

c. Capacitor C₃ by the plate circuit r-1 bypass. The current jack in the plate of tube V³ provides for the plate current measurement nec-

essary for tuning up the power amplifier stage properly.

35. Microphone amplifier.—Resistor R_s is the grid resistor of tube V_s, the first audio amplifier. Resistor R-27 acts as a load resistor for the microphone. Resistor R_s and capacitor C_s act as a decoupling filter for the screen grid of tube V_s. Resistor R_s, also severes to obtain the proper operating voltage on the screen. Resistor R_s is the plate load. Capacitor C_s is a hold-over from the receiver function.

36. Modulator.—e. Capacitor C₁₁ is the coupling capacitor, and R₁₁ is the grid resistor of tube V₂. Capacitor C₂, and resistor R₃₁ make up a decoupling filter for the screen grid of tube V₂. Capacitor C₂₂ provides a low impedance path around the modulation choke L₄ for the current of the carrier frequency. This is necessary as the 4-famplifier tank and modulator choke are in series. The modulator choke L₄ provides a low resistance de- path to the plate of the modulator choke L₄ provides a low resistance de- path to the plate of the modulator choke L₄ provides a low resistance de- path to the plate of the modulator choke L₄ provides a low resistance de- path to the plate of the modulator choke L₄ provides a low resistance and part of the modulator choke L₄ provides a low resistance and part of the modulator choke L₄ provides a low resistance and the provides are chosen to the contract the contract the contract the choke are chosen to the choke are choke a chok

lator and r-f amplifier tubes, and offers a high impedance load to the

b. Resistor R₁₉ prevents overloading the monitoring earphone, as the audio output for modulating the r-f amplifier is quite high. Capacitor C_{2s} removes the d-c at the plate of tube V₃ from the earphones. Capacitor C₁₀ as well as capacitor C₁₁ are B battery BA-38

bypasses.

37. Change-over switch.—The press-to-talk switch operates the change-over switch which makes the necessary circuit changes to convert the set from a receiver to a transmitter. The change-over switch is nade up of 14 sections. Each section has a name which is marked on the calluloid insulating strip covering the change-over switch. For simplicity, however, each section has been designated by a letter of the alumbles of the sebenatic and functional drawings.

(See figs. 3, 4, 16, and 17.)

a. Section A connects the proper crystal into the circuit.

b. Section B connects the voltage divider made up of R₂₃, R₃, and R₃ across resistor R₄ in the receive position, and disconnects the voltage divider in the transmit position. This voltage divider provides the grid bias voltage, for tubes V₁, V₂, and V₂.

c. Section C connects the control grid of tube V₁ to the ave voltage line in the receive position, and connects the control grid to the grid leak risistor R. in the transmit position.

leak risistor R₅ in the transmit position.

d. Section D connects the antenna to the tuning capacitor C₇ in the receive position, and to the plate of the r-f amplifier tube VT-174, in the transmit position.

c. Section E connects the plate of the r-f amplifier tube V₁ to the coupling capacitor C₁₀ of the signal grid of the mixer tube V₂ in the receive position, and connects the plate to the r-f amplifier tank capacitor C₁₀. in the transmit rosition.

f. Section F connects the oscillator feedback control capacitor C₀ to ground in the receive position, and connects capacitor C₆ to the oscillator grid of tube V, in the transmit position.

g. Section G puts the voltage dropping resistor \mathbf{R}_{10} in series with the plate of tube \mathbf{V}_1 in the receive position, and shorts out the resistor

in the transmit position. A. Section H connects the B battery BA-38 to the plate and screen of V, in the receive position, and disconnects the battery in the transmit position. Section H also puts the voltage dropping resistor $R_{\rm tr}$ in series with the plate of tube $V_{\rm tr}$ in the receive position, and shorts out the resistor in the transmit position.

 Section J grounds the microphone in the receive position, thereby eliminating the possibility of pick-up on the microphone being introduced into the audio amplifier. In the transmit position section J connects the microphone to the grid of the first audio amplifier tube

i. Section K in the receive position connects the filament of tube Vz to the A battery BA-37 and disconnects one filament section of each tube VT-174 from the A battery BA-37. Eliminating one filament section of each tube VT-174 reduces the total A battery BA-

37 drain by 100 milliamperes in the receive position.

k. In the transmit position, the filament of tube V, is disconnected from the A battery BA-37 and the second section of the filament in each tube VT-174 is connected to the A battery BA-37. Since one filament is cut out and two are cut in, the drain is only 50 milliamperes higher in the transmit position as compared with the drain in the receive position. I. Sections L and M are tied together electrically through the mov-

ing element of the switch. In the receive position the dropping resistor R16 is placed in series with the screen grid of tube V5 by sections L and M. These switch sections also place the dropping resistor R., in series with the screen circuits of tubes V, and V, and connect the B battery BA-38 to the plate of tube V1. In the transmit position resistors R17 and R16 are shorted out by switch sections L and M

m, Sections N and O are tied together electrically through the moving element of the switch. In the receive position they place the earphone across the audio choke in the plate of tube Vs. and in the transmit position they connect the screen and plate circuits of the r-f amplifier, tube V., to the plate of the modulator tube Vz. This switch section also places the dropping resistor R10 in series with the earphone to reduce the intensity of the signal in the earphone in the transmit position.

38. Description of parts.-a. Resistor-capacitor containers.-On the chassis there are four resistor-capacitor containers which are called cups. These cups fit around the tube sockets and are attached to them with cement. The purpose of the cups is to provide tie terminals and a place for some of the resistors and capacitors used in the set. Each cup consists of a thin bakelite shell of circular shape, with an inner and outer wall. The resistors and capacitors are placed in the space between these walls. Impregnating compound seals these parts into the cup. The top piece joining the two walls is drilled so that the leads from the capacitors and resistors can be brought out. Some of the parts are soldered to terminals riveted to the top piece of the cup. Each cup has a part number marked on it, as well as a schematic

drawing of the parts in it. (See fig. 23.)

b. Antenna coil.—The antenna coil is of the selected type and is word on a polystyrene form. This is a plug-in coil and has three pins on its base. Two of these pins are connected to the coil. The top of each coil is marked with the name, the frequency, and the part number. The antenna coil socket is also of polystyrene, and is fastered to the chassis by a long rivet through its center. This rivet also fastess the antenna chanp and the antenna polystyrene support to the

chassis.

• Plate circuit tank coll.—The tuned r-f amplifier plate coil has been marked TANK and is wound on a small mice filled habelite form.

• Plate from 6 a hexage num 1. The vinding and one are not visible as they are surrounded by a ballelite shell which completely incloses them. This shell is riveted to the coil form. A threaded ballelite serve fits into the threaded iron one, and motion of the scree moves the covered to the winding thready determining the industance covered to the winding thready determining the industance.

(1) In addition to the word TANK the coil is marked with the frequency and the part number. The Signal Corps part number carries the letter C as a prefix to the part number. This identifies it and eliminates confusing it with the frequency numbers. Coil is issued with radio set SCR-538-A are marked with the frequency range and the nart number.

(2) The coil form has a female type base. The coil socket contains two pin connections which fit into boles in the coil form and make electrical contact to the coil. The pins are gripped by spring clip conceins in the base of the coil form. A hole is provided in the socket for the inductance adjusting serves which extends through the form. A spring clip in the socket grips the tuning zerve and provides a more rigid support for the coil. A spring clip not top of the form prevents the coil from weeking loose from the socket.

d. First i-j transformer.—The i-f transformer windings are on a powdered iron core and are surrounded by a powdered iron sleeve to further increase their inductance. This type of construction gives a high inductance with a small winding which results in a small size transformer. The primary and secondary of the first i-f transformer are timed by small adjustable mice trimmers contained in the shield on. The adjustment of the trimmers is reached through two holes in the top of the can. A one megohn resistor is shunted across the secondary winding and serves to broaden the response of the transformer. This resistor is contained in the shield can. The transformer is held in the only a metal bottom pales which is secured by rolling the side walls of the shield over the edges of the plate. Two U-shaped below.

e. Second i-f transformer.—(1) The second i-f transformer construction is similar to that of the first i-f transformer. Only one trimmer is used, however, and it is connected across the secondary winding. This trimmer is accessible through a hole in the top of the shield can.

(2) A 220,000-ohm resistor and two 70-jf-mics capacitors are also mounted in the shield can. The transformer fastens to the chassis in the same manner as the first i-f transformer. They make up an i-f filter for the detector circuit. f. Crystalks.—(1) There are two crystals used in the radio receiver.

of the way we consider the field between the field of the consideration of the field between the frequency than the transmitter crystal. The crystals are contained in plug-in type holden with two pin connections. They are completely sealed against moisture. The receiver crystal holder is plainly marked REC, and the transmitter crystal is marked TRAN. The contract of the contract

(2) The crystal holder has a metal cover plate on which are marked the frequency, crystal namifactures' name, and the melod number. This plate does not make contact with the crystal blank in the holder. This plate does not make contact with the crystal in the scales, the crystal in the scales, the operation of the crystal will be affected. A piece of insulation material covers the chasin where the transmitter crystal might touch when the set is jurned. When the crystal scrivity is low, it touch when the set is jurned. When the crystal activity is low, it is partie, "plate of white properties of the properties of t

MAINTENANCE

Parage	
General.	3
Replacement of batteries	4
Replacement of tubes	4
Replacement of antenna coil	4
Replacement of r-f tank coil	4
Replacement of microphone	4
Replacement of earphone	4
Removal and replacement of crystals	4
Weak signals.	4
No signals	4
Test equipments	4
Test equipment IE-17-(*)	1
Test case CS-S1-(*)	-
Test stand FT-252-(*) and Antenna A-82-(*)	0
Test unit I-135-(*)	t
Presetting frequency with IE-17-(*)	
Removal and replacement of coils and crystals	
Setting up test equipment IE-17-(*)	
Crystal activity test	1
Presetting receiver	-
Presetting transmitter	8
Procedure if badly out of alinement	-
Using signal generator.	6
I-f allnement using test equipment IE-17-(*)	-6
Testing batteries BA-37 and BA-38.	
Test equipment IE-15-A	6
Use of test case CS-S1-(*)	0
Use of test stand FT-252-(*)	6
Test harness and meters	6
Use of test set I-56-(*)	6
Presetting frequency with IE-15-A	6
Changing coils and crystals	3
Setting up test equipment IE-15-A	2
Presetting receiver with IE-15-A	2
Presetting transmitter with IE-15-A	2
I-f alinement	3
Checking for image frequency	2
BC-611-(*) as signal generator.	7
Replacement of parts	3
Trouble location and remedy.	7

39. General.—Maintenance work on this equipment should be done by qualified radio repairmen only. A logical process of checking accessories such as tubes and batteries, when the radio set operates poorly, will often locate the trouble,

- 40. Replacement of batteries.—See paragraph 11a.
- 41. Replacement of tubes.—Remove the chassis from the housing. To do this, unfasten the bottom cover of the housing and remove the batteries. Disconnect the microphone and earphone plugs from the terminal board on the end of the chassis by gently pulling out, Plues and jacks are color coded with small spots of color; green for microphone and red for earphone. Remove the mounting screw in the top cover of the housing, and the chassis can be slid out of the bottom of the housing. Lift the tube retainer bracket at the top of the tube and remove the shield, if there is one. Insert a narrow rod through the bottom center of the tube socket and gently force the tube out. A small narrow-bladed serew driver will be found useful for this purpose. When replacing the tube, be sure it is the right type, that the base of the tube is so turned that the pins fit into the socket properly and are straight. The wide space between pins 1 and 7 of the tube can be used as a guide to line the tube with the socket. (See fig. 10.)
 - 42. Replacement of antenna coil.—See paragraphs 55 and 70.
 - Replacement of r-f tank coil.—See paragraphs 55 and 70.
 Replacement of microphone.—Remove the batteries, card-
- board separator, and chassis from the housing. Then unserew the labelite microphone cover on the housing and the unit on be lifted out of the housing. To detach the microphone unit from the housing, it will be necessary to remove the screw which grounds one of the two leads to the housing. The lead with the connecting plug (green dot), which fits into the jack on the terminal board, is withdrawn through the hole in the housing.
- 45. Replacement of earphone.—The earphone is replaced in the same manner as the microphone.
- Removal and replacement of crystals.—See paragraphs 55 and 70.
 - 47. Weak signals.—If the distance between units in operation is between 100 feet and I mile, and the transmission is poor, the batteries may be weak. The lutteries are designed to give about 15 hours of operation, assuming that the unit is operated for slong periods of time and that the operator is transmitting much of the time. They will last longer if not used contantly. A sign of weak last-teries is a low noise level in the earphone when the set is in the receive position with no incoming signal.
- 48. No signals.—a. If the batteries are placed in the battery compartment, positive end first, the set will not operate. If the batteries are inserted correctly and the set does not operate, the batteries may be dead. Replace them with a new set of batteries.

b. A tube may be burned out or shorted. Remove the chassis from the housing. (See par. 41.) Locate the defective tube and replace it. Reinstall the chassis in the housing. Take care that the chassis fits between the guides provided for it in the case.

c. Make certain that the plate current jumper (fig. 1) is inserted

in its proper place. The set will not operate if this jumper is missing. 49. Test equipments.—The test equipments are designed to simplify testing, frequency presetting and general alinement of radio receiver and transmitter chassis BC-611-(*) which is the heart of radio set SCR-536-(*), IE-17-(*) is an improved version of IE-15-A. The components and method of using both of these equipments is described in the following paragraphs. Either equipment

may be used with all models of radio set SCR-536-(*). 50. Test equipment IE-17-(*).-This equipment consists of the following components:

Antenna A-82-(*), artificial. Test stand FT-252-(*).

Test case CS-81-(*).


Test unit I-135-(*) containing multi-range meter, harness, r-f and a-f oscillators, insulated screw driver, and battery connectors. (This unit combines in one case all the meters and additional equipment required with test equipment IE-15-A.)

51. Test case CS-81-(*) .- As the tuning adjustments are inaccessible because of their location on the chassis, which is covered by the case or housing, a special housing is required to make these adjustments. (See fig. 5.) Test Case CS-81-(*) is similar to the radio set housing except for the holes that have been provided to permit access to the chassis adjustments. This apparatus permits tuning the set under conditions identical to those of normal operation. The presetting adjustments should not be made on the set without the test case being around the chassis, because the set would become detuned when inserted into the regular housing. This detuning or misalinement would result from the additional capacitance introduced into the circuit by the housing.

52. Test stand FT-252-(*) and antenna A-82-(*),-a. The test stand contains clamps to hold the test case and the dummy an-

b. Antenna A-82-(*) comprises a 50-milliampere r-f milliammeter to measure antenna current and a receiver and transmitter dummy antenna consisting of a receive-transmit switch, a 56-ohm resistor, and a variable capacitor of 8 af maximum capacitance.

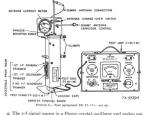55. Test unit 1-135-(")—This unit is a multirange volumeer and milliammetr, a crystal tester, and nr-f and af signal source (fig. 6). Test unit 1-135-(") is used for the measurement of hastery ordegs and current, atmospher place current, author coping voltage, and crystal activity. It is used as a modulated rf-signal source for ing the modulation capability of the transmitter. It combines in one case all the meters and additional apparatus required for test equipment 1E-15-(magnitude or the signal coping or the signal coping or the transmitter. It combines in one case all the meters and additional apparatus required for test equipment 1E-15-(magnitude or the signal coping or the signal copi



of the radio set transmitter crystal such as is contained in radio receiver and transmitter BC-611-(*) or one of the same frequency. It generates a signal of the carrier frequency. This r-f oscillator also serves to check both the receiver crystal and the transmitter crystal for activity.

b. The a-f signal source is a Colpitts oscillator generating a signal of 1,000 cycles per second. This tone is used to modulate the r-f oscillator and can be applied also to the microphone input terminals of the transmitter to test for modulation canability.

573197*-14--4

c. A test harness attached to the test unit provides the means for connecting to the chassis. (See d below.) An insulated screw driver

attached to the cover of the test unit is for alining purposes.

d. Compartments are provided in the test unit for A battery BA-37
and B battery BA-38 to permit these batteries to be tested under load.
(See fig. 7.) Also connections are provided for the use of external
batteries. A heavy-duty L5-volt battery (battery bA-28 or battery
BA-39) and a heavy-duty 90-volt battery (two batteries BA-26 or the voltateries BA-36 or ill be satisfactory for all alliencent and testine

batteries. A heavy-duty 1.6-voit battery (battery B.A.-25 or battery B.A.-25) and a heavy-duty 90-voit battery (who batteries B.A.-26) and a heavy-duty 90-voit battery (who batteries B.A.-26) or two batteries B.A.-36) will be satisfactory for all almenter and testing purposes. Battery B.A.-37 and battery B.A.-38, part of ratio receiver and anomalities B.A.-36 and battery B.A.-38, part of ratio receiver and property of the satisfactory of the

e. The positions of the MASTER SWITCH of the test unit are as follows:

(1) OFF, which disconnects external and internal batteries of test.

(1) OFF, which disconnects external and internal batteries of test unit I-125-(*) from both the test unit and the radio set chassis. The radio set and oscillator are ON in all other positions of the MASTER SWITCH.

(2) BA-37, O-3V. D.C., which indicates on the meter the voltage of external A battery or battery BA-37 when the radio set is in either the receiver or transmit position.
(3) BA-37, O-600 MA, D.C., which indicates on the meter the cur-

rent drain of external A battery or battery BA-37 when the radio set is in either the receive or transmit position.

(4) BA-38, O-150 V. D.C., which indicates on the meter the voltage of external B battery or battery BA-38 when the radio set is in either the receive or transmit position.

(5) BA-38, O-60 MA. D.C., which indicates on the meter the current drain of external B battery or battery BA-38 when the radio set is in either the veceive or transmit nosition.

is in either the receive or transmit position.

(6) PWR. AMP., O-15 MA. D.C., which indicates on the meter the r-f power amplifier plate current when the radio set is in transmit position.

(7) OUTPUT O-60 V. A.C., which indicates on the meter the audio output voltage of the radio receiver; the meter is connected across the earphone in the test unit.

(8) CRYSTAL ACTIVITY, O-1.5 MA. D.C., which indicates on the meter the grid current of the crystal oscillator to show condition of crystal. The MODULATE TESTER switch must be OFF when crystal activity is being checked.

(9) The switch marked MODULATE TESTER is used to modulate the r-f oscillator with a 1,000-cycles-per-second tone when the test unit is to be used for receiver alinement purposes.




f. The switch marked MODULATE TRANSMITTER applies a 1.000-cycles-per-second audio voltage across the microphone input circuit of the transmitter as a test of the modulation capability of the transmitter.

NOTE.-The MODULATE TESTER switch must be ON and a crystal must be in place in the compartment socket when this test is made.

σ. Test unit I-135-(*) also contains an earphone and a microphone which are mounted in the front panel of the case. These can be used to listen to the audio output of the receiver or to modulate the transmitter by speaking into the microphone.

54. Presetting frequency with IE-17-(*).-To cover the authorized range of frequencies from 3.5 to 6.0 megacycles, individual matched sets of antenna coils, r-f tank coils, and crystals are available. Each coil is marked with its frequency and part number so that errors of cail selection will be minimized

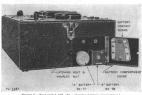

Florus 7.-Test unit I-135-(*)-showing battery compartment.

Norg.—The coils supplied with radio set SCR-536-A are not preset to one frequency. Instead each is adjustable over the small frequency range marked on the coil. The frequency range of each is indicated in chart I (pgr. 70). The coils manufactured for radio sets SCR-536-B and 536-C are identical but have been preset to the frequency indicated on each.

a. To preset the operating frequency of the radio receiver and transmitter BC-611-(*), obtain a coil and crystal equipment of the desired frequency. The coil and crystal equipment comes in an individual carton marked with the frequency and contains the transmitter and receiver crystals, the antenna coil and the r-f tank coil.

Norm.—Badlo sets SCIR-GSF-A are issued with one set of square crystalts. The couli for these radio sets are variable in the frequency ranges indicated in chart (par, 70). Radio set SCIR-GSF-B is issued with only one set couls and crystals. Radio set SCIR-GSF-B is insued with only one set could not crystals. Radio set SCIR-GSF-B is insued with only one set couls are described in the CSF-GSF-B in the could be could


b. The antenna coil is larger and of different shape than the r-f tank coil. Its base connections also differ, so it is impossible to put the coils in the wrong sockets. Both coils are of the plug-in type. (See figs. 8 and 10.)

a. Remove the chassis of radio receiver and transmitter BC-611-(*) from its housing. To do this, unlatch the bottom cover of the housing and remove the batteries. Place them saids for text. Disconnect the microphone and earphone plugs from the terminal board on the end of the chassis by gently lifting them up. Next remove the screw in the top cover of the housing; the chassis then will slide out of the bottom end of the housing.


55. Removal and replacement of coils and crystals.—a. Antenna coil.—Remove the plug-in antenna coil by carefully lifting it out of its socket. See figure 10 for its location. In its place insert another coil of the desired frequency.

b. Bf tank oul.—To remove, loosen the screw holding down the screw holding down the spring free of the coil. See fig. 6). Swing the spring free of the coil. The coil then can be lifted out of the socket. When replacing with another coil of the desired frequency, carefully fit the coil over the two pins projecting up from the socket so that the fill into who holes in the coil from and the coil adjustment sharf find into the holes in the coil from and the coil adjustment sharf replace the coil ratio the score principle of the coil, and tighten the serve holding the spring.

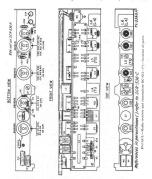c. Orystok.—The crystals are mounted in plug-in type holders. (See fig. 10.) To remove a crystal, lift up the chanp located on top of the crystal holder. This champ pivots on a stud fastened to the chassis. Place a small serew driver between the crystal holder and the scoket and gently pry it up. To remove the other crystal holder to the same procedure is followed. Select a transmitter and a receiver crystal holder of the desired frequency (the frequency of the transmitter and a receiver crystal will be 450 ke higher in frequency). Insert he receiver crystal will be 450 ke higher in frequency). Insert he receiver crystal will be 450 ke higher in frequency). The reserved crystal will be seen and the crystal value for the crystal value f arrow on the holder points in the same direction as the arrow on the socket. When the transmitter crystal is inserted, place it in the socket marked TRAN, in exactly the same way. The printed metal



side of the holder should show through the opening in the chassis, Honever, do not insert the transmitter crystal in the radio set at this time. Instead, replace the metal clamp on the receiver crystal holder on the chassis and leave the transmitter crystal socket empty.

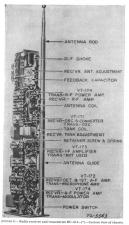

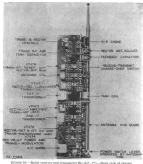


FIGURE 10.—Radio receiver and transmitter BC-611-(*)-front view of chassis.

56. Setting up test equipment IE-17-(*) .- a. Place the chassis into test case CS-81-(*) housing. The chassis must be inserted into the test case through the bottom as is done when inserting the chassis into its own housing. Take care that the chassis fits between the guides provided for it in the case. It should not be necessary to force the chassis. If force is necessary, withdraw the chassis and check to see that no parts are catching on the test case or that the chassis has not jumped the guides. Slip the top cover over the antenna rod and fasten the chassis to it with the knurled mounting screw. The chassis now will be held securely in the test case. Now remove the plate current meter jumper from the terminal board at the bottom end of the chassis.

Caution: Do not misplace this jumper since it must be replaced

after alinement tests.

5. Attach the terminal board of the I-135-(*) harness to the terminal board of the chassis so that the two mall pins on the harness terminal board fit into the plate current meter jacks, and that the two large locking pins, one on each end of the terminal board, it into the holes provided for them. Lock the two terminal boards to gother by a sideward movement of the levers attached to the locking pins.

c. Next, clamp test case GS-81-(*) into test stand FT-929-(*) with the antenna end up, and the housing in such position that the change-over switch is opposite the left side of the operator as he faces the stand. (See fig. 5.) The upper clamp should grip the housing on the edges of the top cover. The lower clamp should not be

made too tight, as the pressure may crack the housing.

d. Make certain that the MASTER SWITCH of test unit

L-13a-(*) is in the OFF position. Place the transmitter crystal holder of the desired frequency in the crystal seeks in the trout panel compartment of test unit 1–135-(*). (See fig. 6). Be sure the crystal is of the same frequency as the coils in the radio set and that its frequency is 460 to law than the receiver crystal. Commodification of the control of the co

97. Crystal activity test.—He sure that the transmitter crystal has been properly placed in the crystal secket of the test unit. Place the MODULATE TESTER writch in the OFF position than the MAPTER SWITCH were the MODULATE TESTER witch in the OFF position that the MAPTER SWITCH were a land 8 milliamperes. If the many the many that the control of the many that the caternal battery voltages applied to the test unit 1-135.—If it reads less than 3 milliamperes the crystal for poor activity, be sure that the external battery voltages applied to the test unit 1-135.—If the proper test applies of the read is and 90 voltages applied to the set unit 1-135.—If the proper test applies of the region of the proper frequency in place in test unit 1-135.—If yet provider frequency presenting adjustments.

58. Presetting receiver.—Use the following procedure:

a. Extend the radio set antenna rod to its full length, 39 inches above the top cover of test case CS-81-(*). This will turn on the radio set. Do not press the press-to-talk switch of the test case during the receiver presetting adjustments.

b. Before proceeding with the necessary set adjustments, check operating voltages and currents, using the multirange meter of test unit I-125-(*). The following voltage and current readings are

normal:				t readings are		
Master switch set at.	BA-37 0-3 V. D. C.	BA-37 0-600 MA, D, C.	BA-38 0-150 V. D. C.	BA-38 0-60 MA. D. C.		
Motor should said	1 97 (ara		1000		

1 Replace batteries if voltage is less than minimum flaure.


c. The receiver is now ready for alinement. Be sure that a good transmitter crystal of the proper frequency is in place in the test unit. The preceding activity check of the transmitter crystal will assure that a radio-frequency signal is being generated.

d. Turn the MASTER SWITCH to OUTPUT, 60 V. A. C., position. A reading should now be indicated on the meter and a 1,000-cycles-per-second tone should be heard in the earphone of the test unit.
e. Set the MODULATE TESTER switch to ON. The 1,000-

cycles-per-second tone will now modulate the carrier signal.

f. Grasp the test case with one hand during the following alinement adjustments on the receiver.

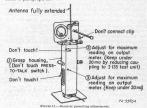g. The location of the receiver tuning adjustments on the radio chassis are shown in figures 5 and 11. With the insulated serves driver, turn the receiver antenna adjustment serves tockwiss. Notice the effect of this adjustment on the output meter reading, If the meter reading increases, continue to tighten the serve until a maximum reading is obtained. If the reading decreases, turn the serves counter-fockwise until a maximum reading is obtained. Be careful not to lighten the screw after it begins to turn hard as the threaded base of the trimmer will be stripped. The setting of the trimmer screw for maximum output should fall somewhere between the point of hard tuning and that of minimum pressure. If the maximum is not reached in these limits of the screw adjustment, try another antenna coil. If the set appears to be badly out of alimement, proceed as indicated in neuronam 60.



Nors.—Be sure that the rf signal is not strong enough to cause overlocaling the receiver. If this condition exists, adjustment of the receiver antenna trimmer will have little or no effect on the output reading. Best results will be obtained if the rf input is adjusted so that the meter reading on the 60-voit scale does not exceed 10 voits, although satisfactory results may be obtained with readings up to 20 voits.

h. Using the insulated screw driver, turn the receiver tank adjustment screw for maximum output using the same method employed in step g above.

Norm—This server, which is made of baloilite, file into a produced iron one which is threaded. The novement of the server disappes the position of the over in the coil. If the server is turned too far clockwise, the core will ride use all the server beard, and the threads in the core will be stripped. If the server is turned into far countercolockwise, the core will come in contact with the colle socket, and further turning will again strip the core threads. The serve settling for maximum output should full somewhere between these two limits of adjustment. If it does not, a wrong tank coll may be in the adjustment of the close not, a wrong tank coll may be in the adjustment.

i Turn the MASTER SWITCH to OFF. Remove the transmitter crystal from test unit I-135-(*). Telescope the rod antenna and remove the test harness and the knurled fastening screw from the chassis in the test case. Then slide the chassis out of the test case and remove the receiver crystal and install it in I-135-(*) test unit. Insert the transmitter crystal in its proper socket in the radio set, making sure it is properly installed, and put the chassis back in the test case. (See par. 55.) Attach top cover and the harness terminal board. Put test case in place on the test stand. Then test the receiver crystal for activity in the same manner as for the transmitter crystal (par. 57). Leave a good receiver crystal in place in the test unit while presetting the transmitter portion of the radio set.

59. Presetting transmitter .- a. Grasp the test case and depress the press-to-talk switch with one hand during all following presetting adjustments of the transmitter. The MODULATE TESTER switch should be OFF unless otherwise specified.

b. Extend the antenna of the radio set to its full length. This will operate the power switch in the radio set chassis.


c. Before proceeding with the necessary set adjustments, check opcrating voltages and currents; using the multirange meter of test unit I-135-(*). The following voltage and current readings should be obtained with press-to-talk switch on the radio set depressed;

Master switch set	{ 0−3 V. D. C.	BA-37 0-600 MA. D. C.	BA-38 0-150 V. D. C.	BA-38 0-60 MA. D. C.
Meter should read.	1.35 (min.) ¹ to 1.5 v.	275-300 ma.	75 v. (min.) ¹	26-30 ma
	name to have them the unitains	nes formes		

d. The transmitter is now ready for alinement. Turn the MAS-TER SWITCH on test unit to PWR, AMP, position. Adjust the transmitter tank adjustment screw for minimum current reading on the meter in the test unit. The normal reading in this position is approximately 7 milliamperes. See figures 5 and 12 for location of transmitter tank adjustment. Be sure to depress the press-to-talk switch with one hand during this operation.

e. Telescope the upper three sections of the antenna rod, leaving only the bottom or fourth section fully extended from the housing, Clip the dummy antenna connection to the upper part of the antenna rod. (See fig. 12.) Set the antenna change-over moitch on the panel of test stand FT-252-(*) to TRANS, position, and then, still

grasping the test case and press-to-talk switch, use the insulated shaft extension to adjust the duman outenon conscious control for minimum, corrent realing on the meter in test until I-155-(*) (appminimum, corrent realing on the meter in test until I-155-(*) (apption). The control is a supplied by the control is necessary to compensate for the change in antenna expantance due to telescoping the upper three sections of the antenna rodcloserve the reading of the antenna convent matter on test stand. Observe the reading of the antenna convent matter on test stand to the control is the control of the control of the control of the control of the Part 252-(*). This should be from it to 24 millianspers and repre-

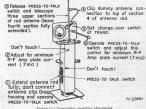

un 12.—Transmitter presetting adjustments.

f. (1) Place the MODULATE TESTER which to ON position and press the MODULATE TRANSMITTER, lattors on the test unit. This modilates the transmitter by applying, a 2-volt, 1,000-cycles-persond audio signal across the microphose terminats. Note the rise in the antenna current meter reading where the modulated signal is applied. This rise should be at least of perent over the unmodulated current reading. A 6 persont increase in antenna current indicates to percent uncellulation. For example, assume that the unmodulated current reading.

antenna current is 20 milliamperes and that the modulated current is 22 milliamperes:

The increase in current is then

22/20=2 milliamperes;

The percentage increase will be

2/20×100=10 percent.

(2) Another method is to divide the antenna current obtained

with modulation by the antenna current without modulation; the answer should be greater than 1.06. For example, take the values of current previously given. Dividing the modulated current by the unmodulated current gives 22/20-1.10.

Note.-Further checks on modulation may be made by whistling into the microphone or holding a sustained note. The modulation rise should be substantially greater. MODULATE TRANSMITTER button must not be pressed when using the microphone method.

g. This completes normal frequency presetting adjustments. Remove the chassis from the test case, replace in the radio set housing and reconnect microphone and earphone. Be sure to replace the plate current meter jumper. Reinstall the A and B batteries, making certain that the positive (+) ends face outward. Close the cover, move the latching bolt into place, and tighten the knurled nut. The set is now ready for operation.

60. Procedure if badly out of alinement.-If the i-f transformers are badly out of alinement, it may be impossible to get a carrierfrequency signal through the receiver as outlined in paragraph 58. For such a condition, the i-f transformers must be realined. There are two ways of doing this, one way being to use a 455-kc signal generator connected to the signal grid of the mixer tube, while the second method makes use of test equipment IE-17-(*).

61. Using signal generator .- a. Remove the chassis from the test case and with the mounting screw fasten it to the top cover of the housing. Place the chassis in the test stand in the same relative position as when in the test housing, and hold it there by gripping the housing cover with the upper clamp of the test stand. (See fig. 13.) Leave test unit I-135-(*) connected to the chassis by means of the harness.

b. Connect the ground lead of the signal generator to test stand FT-252-(*). Connect a .05-af capacitor in series with the output lead of the signal generator and connect the other end of the canacitor to the No. 6 pin of tube VT-171, used as a converter-oscillator. Set



FIGURE 13.—Servicing set-up with test stand PT-252-(*).

the signal generator frequency accurately to 460 ke by means of frequency meter set SCR-291-(*). Set the MASTER SWITCH of the quency meter set SCR-291-(*) could be set of the Master Street of the test unit to OUTPUT 0-60 V. A. C. position. Do not depress the test unit to OUTPUT 0-60 V. A. C. position. Do not depress the press-to-talk switch. Adjust the generator output until a 10-witch. Adjust the generator output until a 10-witch with the required when the set is badly out of aliencent.

c. Adjust the trimmer on the second i-f transformer for maximum andio output. Do not grasp the test stand during i-f alinement. Reduce the generator output as the audio output increases above 10 volts. Next, peak the secondary on the first i-f transformer, and then peak the primary trimmer. After these adjustments have been made, put the chassis back into test case CS-81-(*) and aline the set as desertled in presetting receiver procedure, paragraph 5.


62. Lf alinement using test equipment IB-17-(*)—a. 8 sure that the frequency of the REC (receive) cystal is 458 is higher than that of the TRANS (transmitter) crystal. The chassis may be left in the test case when using this method. The receiver crystal must be installed in the chassis and the transmitter crystal in the test unit I-133-(*).

b. If the presetting receiver procedure described in paragraph 88 has been followed, and no readable audio voltage has been obtained on the OUTPUT 0-00 V. A. C. position of the test unit meter, first make sure that a maximum rf signal is being radiated. This can be assured by connecting a short length of wire to the R. F. OUTPUT terminal of the test unit and placing this wire close to the receiver antenna.

Norg.—Test unit I-135-A does not have an R. F. OUTPUT terminal. The instructions furnished with the unit explain how to make this connection.

c. With the MASTER SWITCH of the test unit on OUTPUT 50 V. A.C. (modulate tester witch 0.0), adjust the second 1-f secondary trimmer for maximum output, next the first 1-f secondary trimmer for maximum output, next the first 1-f secondary trimmer and the first 1-f primary trimmer last. (See fig. 5.) All 1-f trimmers are adjusted for peak output meter reading. As the 1-f trimmers are adjusted to peak output meter reading. As the 1-f trimmers are almed, toosen the signal complete the receiver antona so the maximum audio output reading of the meter is not over 10 vots. This is necessary to prevent overshould the reactive and consequent that the performed very carefully for good results. Go over the allienmust be performed very carefully for good results. Go over the allienments a coord dime.

d. After the i-f alinement adjustments have been made, complete the procedure by adjusting the receiver antenna adjustment series and the receiver tank adjustment as described in paragraph 580 and h. 65. Testing batteries BA-37 and BA-38.—a. Use test equipment IE-17-C/10 rish test, but he use that the external heavy-duty batteries are disconnected. The radio set chasis with both expenditure batteries are disconnected. The radio set chasis with both expenditure batteries are disconnected. The radio set chasis with both packed in the test stand with antenna cel extended. The press of salk excited must be in tensamily position. The MASTER SWITCH of the truth should be OFF. Place radio as batteries BA-37 and BA-38 in the compartment of the test unit. Close and secure the compart. OFF.

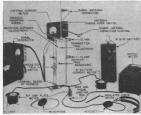

Prount 14.—Test equipment 1E-I5-A-set up.

b. Place the MASTER SWITCH on test unit in BA-37, O-3 V. D. C. position and observe the meter reading. Normal readings will be between 1.85 and 1.5 volts. If the voltage is less than 1.25 volts, the battery should be discarded and replaced with a new one.

c. Place the MASTER SWITCH on test unit in BA-88, O-150 V. D. C. position and observe the meter reading. Be sure the set is in transmit position. The normal meter readings will be between 75 and 103.5 volts. If the voltage is below 70 volts the battery should be discarded and replaced with a new one.

41

d. When it becomes necessary to discard battery BA-37 or battery BA-35 because of low voltage, both batteries in the radio set should be replaced at the same time. Batteries which are near the lower voltage limit may be used, but they will reduce the overall performance of the radio set.

64. Test equipment IE-15-A.—a. The purpose of this test equipment is identical to that of test equipment IE-17-(*). Test equipment IE-15-A consists of the following components:

Test stand FT-252-A, including dummy antenna and r-f

Test case CS-81-(*) Milliammeter, O-50, d-c Milliammeter, O-15, d-c

Harness
Feedback capacitor

b. The following additional equipment is required when using test equipment IE-15-A: R-f signal generator

R-f signal generator Test set I-56-(*) Frequency meter SCR-211-(*)

Battery supply (BA-40) Microphone

Headset Insulated tuning screw driver

Small zerow driver

Small zerow driver

Small zerow driver

Small zerow driver


Interesting because of their locations con
the classic being covered removable because of their locations con
the classic being covered removable making these adjustments. (See
fig. 14) Test case CS-St-C') used for this purpose, is similar to a
classic bosing except for the holes that have been provided to permit
conditions identical to those of normal operation. The tuning adjusment abould not be made on the set without the test case housing
around the chanels, because the set would become detuned when inconditional experience introduced into the circuit by the spatial from the
additional experience introduced into the circuit by the spatial from the
additional experience introduced into the circuit by the spatial from the

66. Use of test stand FT-282-(*).—This test stand contains clamps to hold the test case CS-SI-(*) or the radio set chassis, a 29-milliamper -f meter to measure transmitter antenna current, and a receiver and transmitter dummy antenna consisting of a receiver-transmit switch, a 36-ohm resistor, and a variable capacitor of ceiver-transmit switch, a 36-ohm resistor, and a variable capacitor of

8 μμf maximum capacitance.

67. Test harness and meters.—A special test harness cord supplied with the stand provides connections for the batteries, rf amplifier plate current meter, total B current meter, audio output meter, earphone, and microphone. The schematic drawing of this harness is shown in figure 15. The 10-milliampere meter is used to measure used to measure the connections to the total B lattery BA-38 surrent. The terminal board stateded to the harness provides a simple method of making the connections to the chassis.

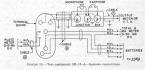68. Use of test set I-58-(*).—Since radio receiver and transmitter BC-611-(*) output is designed to operate into a high-impedance earphone, the output meter provided in test set I-58-(*) is un-



satisfactory for alinement purposes because of its low internal resistance. This output meter has a resistance of only 4,000 olmus. A vacuum tube volteneter with a minimum input impedance of 10 sealestive analyzer test at 1-5e-0°, have a satisfactory output meter if the 20-volt ac range is used. Since the meter sensitivity is 1,000 dana per volt, 20,000 olmus is placed across the receiver output when with the AC output meter is necessary to prevent the B battery and the contract of the con

69. Presetting frequency with IE-15-A.—To cover the authorized range of frequencies from 3.5 to 6.0 megacycles, individual matched sets of antenna coils. r-f tank coils, and crystals are avail-

able. Each coil is marked with its frequency and part number so that errors of coil selection will be minimized

Norz.—The coils supplied with radio set SCR-535-A are not preset in one frequency. Instead, each is adjustable over the small frequency range marked on the coil. The frequency range of each is indicated in chart I. The coils manufactured for radio sets SCR-535-B and SCR-536-C are identical but have been preset to the frequency indicated on each.

a. To preset the operating frequency of radio receiver and transites Bc-411-(*), obtain act oil and crystal equipment of the desired frequency. The coil and crystal equipment comes in an individual carton marked with the frequency and contains the transmitter and receiver crystals, the antenna coil, and the r4 tank coil. The satema coil is larger and of different shape than the r4 tank coil. He base connections that of the different shape than the r4 tank coil. In base connections that of the different shape the plays the part of the plays to produce the coils in the and 100.

b. Remove the classis of radio receiver and transmitter BC.-611.-(*) from its housing. To do this, unlatch the bottom cover of the housing and remove the batteries. Place them saids for test. Disconnet the microphone and earphone plugs from the terminal board on the end of the chassis by gently lifting them. Remove the screw in the top cover of the housing; the chassis then will slide out of the bottom end of the chousing;

70. Changing coils and crystals.—a. Antenna coil.—Remove the plug-in antenna coil by carefully lifting it out of its socket. See figure 10 for its location. In its place insert another coil of the desired frequency.

b. Rf. took coll—To remove, loose the screw holding down the collectance spring on top of the coll. (See fig. 3). Swing the spring free of the coil. The coil then can be lifted out of the socket. When the collectance is the collectance of the desired frequency, carefully fit the coll over that two districts of the collectance of th

(See fig. 10). To renove a cyr diolined in plug-in type inonexts. (See fig. 10). To renove a cyr diolined in top of the cyrstal holder. This closup picture declared in top of the cyrstal holder, and the cyrstal holder in the seeket and gently pry it up. To remove the crystal holder and holder in the seeket and gently pry it up. To remove the other crystal holder, the same procedure is followed. Select a transmitter and a receiver exystal holder of the desired frequency. (The frequency of the trans-


mitter crystal will be the same as that of the coils, while the receiver crystal will be 55 be higher in frequency. I meet the receiver crystal holder in the crystal secket marked ERC. It should be inserted so that the frequency printed on the metal side faces out and the arrow on the holder points in the same direction as the arrow on the socket. Place die transmitter crystal in the socket marked TRA, in exactly the same way. The printed metal side of the holder should show through the opening in the classis:


CHART L-Frequency range of coils for radio set SCR-538-4

R-F Tunk	Frequency (in ke)	Antenna	Frequency (in ke)
C-370	3500-3825	{C-358 C-359	3500-367 3675-382
C-371	3825-4225	(C-360 C-361	3825-402 4025-422
C-372	4225-4625	C-362	4225-442 4425-462
C-373.	4625-5075	C-364	4625-482 4825-507
C-374	5075-5500	C-366 C-367	5075-530 5300-550
C-357	5500-6000	C-368 C-369	5500-577 5775-600


71. Setting up test equipment IE-11s-A.—a. Connect the four wires of the harms marked A+, A-, B+, B-, to their proper terminals on the latteries. Connect the two wires marked VT-13t In the control of the control of the control of the control of the two wires marked TO/LM. Set of the control of the control of the selective analyzer two unmarked wires to the 3o-voil s-crange of the selective analyzer unit of test set 1-56-(*). Connect the earphone to the terminals marked G and P on the junction box attached to the harmes. The explosure land connected to the braided shield should connect to the explosure land connected to the braided shield should connect to the

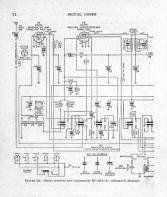b. Thee the clausis into the test housing. The clausis must be inserted into the set housing through the bottom, at is done when inserting the clausis into its own housing. Take care that the clausis into its own housing. Take care that the clausis find between the guides provided for it in the housing. It should not be necessary to force the chassis. If it is, withdraw the clausis and check to see that no parts are catching on the housing or that the classis to the visit of the 30° morning server. The chassis then will be held securely in the test housing. Now creame the plate curvent note; pumper from the terminal bound at reasons the first curvent notes promper from the terminal bound at




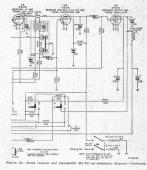

47

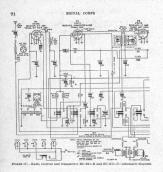



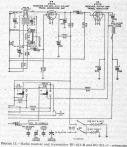

diagram—Continued,

Caution: Do not misplace the jumper.

c. Attach the terminal board of the harness to the terminal board of the chassis, so that the two small pins on the harness terminal board fit into the plate current meter jacks, and so that the two large locking pins, one on each end of the terminal board, fit into the holes provided for them. Lock the two terminal boards together by a sideward movement of the levers attached to the locking pins.

d. Next clamp the test housing into the test stand FT-252-(*) with the antenna end up, and the housing in such position that the changeover switch is opposite the left side of the operator, as he faces the stand. (See fig. 11.) The upper clamp should grasp the housing on the edges of the top cover. The lower clamp should not be made too

tight as the pressure may crack the housing.

c. The signal generator used should be modulated 30 percent by a 400 to 1,000 cycles per second tone and should be accurately set to the carrier frequency of the radio receiver and transmitter BC-611-(*). The signal generator frequency must be checked with an accurate frequency meter, such as SCR-211-(*).

72. Presetting receiver with IE-15-A .- a. Extend the radio set antenna rod to its full length, 39 inches above the top cover of test case CS-81-(*). This will turn on the radio set. Do not press the press-to-talk switch on the test case during the receiver presetting

adjustments.

b. Connect the ground lead of the r-f signal generator to the test stand, but leave the output lead of the signal generator unconnected. The r-f input to the receiver will then be the pick-up on the antenna. The generator output should be adjusted for a reading of approximately 10 volts on the 50-volt a-c range of the output meter. If the receiver is badly out of alinement it may be impossible to get this output reading or any at all; in such a case follow procedure in paragraph 74.

c. Grasp the test case with one hand during all of the following

adjustments.

d. The location of the receiver tuning adjustments is shown in figures 11 and 14. With the insulated screw driver, turn the receiver antenna adjustment screw clockwise. Notice the effect of this adjustment on the output meter reading. If the meter reading increases, continue to tighten the screw until a maximum reading is obtained. If reading decreases, turn the screw counterclockwise until a maximum reading is obtained. Be careful not to tighten the screw after it begins to turn hard as the threaded base of the trimmer will be stripped. The setting of the screw for maximum output should fall somewhere between the point of hard turning and that of minimum pressure. If a maximum point is not reached in these limits of the screw adjustment, try another antenna coil. If the set appears to be badly out of alinement, follow procedure in paragraph 74.

Norm—the sure that the rf signal is not strong enough to cause overfooding of the receiver. If this condition exists, adjustment of the receiver antenna adjustment serve with have little or no effect on the output reading. Best results like obtained if the rf output from the signal generator is adjusted, so that the output never reading on the 50-voit acc scale does not exceed 10 vists, atthough satisfactory results may be obtained with readings up to 20 vists.

c. Using the insulated screw driver, turn the receiver tank adjustment screw for maximum output, using the same method employed in paragraph 72d.

Norm.—This serves, which is made of bakelits, fits into a powdered free core which is threaded. The novement of the server changes the position of the core in the coil. If the serve is turned too far clockwise, the core will ride up against the serves bend, and the threads in the core will be striped. If the serve is turned too far continerichekwise, the core will come in contact with the server is turned too far continerichekwise, the core will come in contact with the server is turned too far continerichekwise, the core will come in contact with the server is server to be served in the server is contact to the server in the server is contact. It is does not, a wrong tank coil may be in the set. This completes the receiver adjustments.

73. Presetting transmitter with IE-15-A.—a. Grasp test case and operate press-to-talk switch with one hand during all the following presetting operations to the transmitter:

(1) Using the small screw driver, adjust the transmitter task adjustment screw for minimum current reading on the 15-milliampere meter. The normal reading is approximately 7 milliamperes. See figures 12 and 14 for location of the transmitter task adjustment.

screve. Release the press-to-talk switch.

(2) Telescope the upper three sections of the antenna rod, leaving only the bottom or fourth section fully extended from the housing. Next, clip the dummy antenna connection to the upper part of the antenna rod, (See fig. 12.) Set the antenna chance-over switch

on the panel of test stand FT-252-(*) to TRANS, position.


(3) Connect the microphone provided with the test set to the M and G terminals of the test harness. The braided lead goes to the G


terminal.

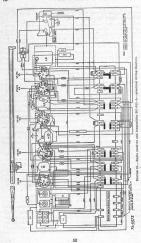(4) Grusp the test case and depress the press-to-talk switch again.

Using the insulated shaft extension, adjust the dummy antenna capacitar control for minimum current reading on the 15-milliampere

meter. The reading should be approximately 7 milliamperes. This adjustment of the dummy antenna capacitance for minimum power amplifier plate current is necessary to compensate for the change in antenna capacitance due to telescoping the upper three sections of the



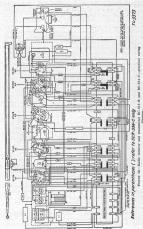

The two leads have been removed from the dummy lugsat Section "L" and moved to dummy lug between Sections "G" and "L" on the receive-transmit switch.

antenna rod. Observe the reading on the antenna current meter on test stand FT-252-(*). It should be from 15 to 24 milliamperes,

representing the unmodulated antenna current.

(5) (a) Modulate the transmitter by whistling a steady note into the microphone, and watch the antenna current nater on the stand. It will be found that the noter reading increases. Keep whistling until the pointer on the nater weeking increases. Keep whistling with the control of the co

24-20-4 milliamperes

the percentage increase will be:

4/20×100=20 percent

(6) Another method which can be used is to divide the current when whistling by the current when not whistling. The answer should be greater than 1.15. For example, take the values of r-f current previously given. Dividing the modulated current by the unmodulated current gives 34/20=1.9.

b. If less than 15 percent increase is obtained, check the crystal for activity; and also check the modulator, r-f amplifier, and oscillator tubes for output. Be sure that the battery voltage under operating

conditions is at least 75 volts.

c. This completes normal frequency presetting adjustments. Remove the classis from the test case, replace it in the radio set housing, and reconnect the microphone and earphone. Be sure to replace the plate current meter jumper. Reinstall the A and B batteries, making certain that the positive (+) ends face out. Close the cover, move the latching boll into place, and tighten the knurrled nut. The set is now ready for operation.

74. I-f alinement.—If the i-f transformers are badly out of alinement, it may be impossible to get a carrier frequency signal through the receiver as outlined in the presetting receiver procedure. For such a condition, the i-f transformers should be realined. Use the

following procedure:

a. Remove the chassis from the test case and fasten it to the top cover of the housing with the mounting screw. Then place the chassis in the test stand in the same relative position as when in the test hous-

from the dimens high I Section "L" and moved to duminy king between Sections "G" and "J" on the receive-frankfull

ing, and hold it there by gripping the housing cover with the upper clamp of the test stand. (See fig. 13.)

b. Connect the ground lead of the signal generator to the test stand FT-252-(*). Connect an .05-µf capacitor in series with the output



lead of the signal generator, and connect the other end of the capacitor to the No. 6 pin of the tubs YI—T1. Set the signal generator ending the quency to 458 ke and then adjust the generator output until a 10-volt reading is obtained on the 50-volt ac-range of the output meter. On siderable generator output will be required when the set is badly out c. Adjust the trimmer on the second i-ft transformer for maximum output. Reduce the generator output as the output increases above 10 volts. Next peak the secondary trimmer on the first i-f transformer, and then peak the primary trimmer. After these adjustments have been made, put the chassis back into the housing and aline the set as given in the presenting receiver procedure. (See fize. 5)

75. Checking for image frequency—a, General,—When setting the generator frequency, care must be taken that the frequency is that of the signal to be received and not the image frequency, which is exactly 910 ke higher than the carrier frequency. For example, a unit alimed for proper operation at 4,000 ke will have an image response at 4,910 ke, while one which operates on 5,000 ke will have an image response at 5,000 ke.

b. Image frequency check.—In checking for proper operation (in regard to image reception) take the following steps: (1) Completely aline receiver to the carrier frequency. Note the

 Completely aline receiver to the carrier frequency. Note the signal generator dial reading.
 Refer to the calibration charts of the signal generator (or to its

(2) Refer to the calibration charts of the signal generator (or to its dial if it is directly calibrated) and estimate the dial reading for a frequency of 910 kc above that in the step (1) above.
(3) Increase signal generator output to 1,000 times its output nec-

(3) Increase signal generator output to LOOD times its output necessary to produce in Ovde across the explanes and the output neter, exactly to produce in Ovde across the explanes are considered in step (2) above. A signal should now be heard. Rotate the sink of on amaximum signal as indicated on the output neter. Adjust the generator output by means of the attenuator so that the output neter across the explose indicates exactly 10 volts. Not the reading necessary to produce 10 volts. If this image frequency sensitivity is doubt a result of the reading necessary to produce 10 volts. If this image frequency sensitivity is doubt a result of the reading necessary to produce 10 volts. If this image frequency sensitivity is doubt a result of the reading necessary to produce 10 volts. If this image frequency sensitivity is doubt a result of the reading necessary to produce 10 volts. If the reading necessary to produce 10 volts are not one of the reading necessary to produce 10 volts are not one of the reading necessary to produce 10 volts are not one of the reading necessary to produce 10 volts. The reading necessary to produce 10 volts are not one of the reading necessary to produce 10 volts. The reading necessary to produce 10 volts are not one of the reading necessary to produce 10 volts. The reading necessary to the carrier frequency it is a certainty that the receiver is not correctly interesting necessary to the carrier frequency in the reading necessary to the carrier frequency of the reading necessary to the reading

76. BC-911-(*) as signal generator.—a. General.—(1) If a situation should arise in which it is necessary to change the frequency of radio receiver and transmitter BC-911-(*), and no signal generator is available, it is possible to preset the frequency provided another radio receiver and transmitter BC-911-(*) operating at the same carrier frequency is available.

(2) If another such set is available, but is not of the correct carrier frequency, it can be made to operate at the correct frequency by inserting the correct crystal and proper antenna and tank coils.

(3) In order to preset one set, it will be necessary to convert the other set into a modulated signal generator. This may be done by simply putting the set in the transmit position and placing a buzzer near the microphone; if a buzzer is not available, the carrier can be self-modulated by converting the audio amplifier in the set into an audio oscillator. This circuit change can be made easly by placing a canacitor of 100 puf between the microphone plug and the plate current meter jack on the terminal board of the chassis. This capacitor will provide enough feedback between the input and output to cause the audio amplifier to go into oscillation. When the radio set is put into the transmit position, an audio note will be heard in the earphone of the unit and a signal will be radiated, modulated by this audio tone. A special capacitor designed for this purpose is supplied with test equipment IE-15-A. (See figs. 21 and 22.) To simplify connections, one lead of the capacitor is tipped with a spade lug and the other lead is tipped with a plate current meter jumper. The snade lug has a small hole in it for the microphone plug and is designed to fit between the microphone plug and the microphone tack on the terminal board. The spade lug is painted green to identify it with the microphone plug, which is marked with a green spot.

(4) The plate current meter jumper connected to the capacitor replaces the plate current jumper in the set.

b. Setting up the signal generator .- Procedure for converting radio receiver and transmitter BC-611-(*) into a modulated signal generator is as follows:

(1) First remove the chassis from the housing of the set, (2) Select a crystal of the exact frequency to which the other set

is to be preset, and place it in the transmitter crystal socket. Select

another crystal which is 455 kc higher in frequency and place it in the receiver crystal socket. Select the proper antenna and tank coils and insert them into their respective sockets.

(3) Place the set into the test housing and connect the test harness as described in paragraph 71.

(4) With the antenna rod fully extended, grasp the test case and put the set in the transmit position and with a small screw driver adjust the transmitter tank adjustment screw for minimum reading of the plate current meter.

(5) Disconnect the harness from the chassis and remove the chassis from the test housing. Do not forget to replace the plate current meter immer. Put the set into its own housing and connect in the audio feedback capacitor. (See figs. 21 and 22.) Place the spade lug of the capacitor lead between the microphone jack and the micro-





PICTUS 22.—Placement of audio feedback caracitor.

55

www.ehortwaveredin

phone plug. Remove the plate current meter jumper and replace it with the jumper attached to the other capacitor lead. Replace the batteries and place the capacitor into the space between the housing wall and the B battery spacer and then close the bottom cover. Check the set to see that it is oscillating by operating the press-to-talk switch and listening for an audio tone. The set is then ready for use as a modulated signal generator.

e. Presetting the set .- (1) Remove the chassis from the housing of

the set to be preset and insert the correct crystals and coils.

(2) Put the chassis into the test housing and attach the test harness; then extend the antenna to its full length. Do not connect the dummy antenna,

(3) Tie down the press-to-talk switch of radio receiver and transmitter BC-611-(*) being used as the signal generator, with a piece of twine or wire, place it about 20 feet away from the receiver to be preset and extend its antenna.

(4) With the set in the test case in the receive position, adjust the automax trimmer for maximum andious output. If the signal picked natural relations of the property of the receiver another and the receiver another and observed the receiver another anoth

(5) Next adjust the receiver tank adjustment screw for maximum audio output. The receiver is now properly alined and the radio receiver and transmitter BC-611-(*), used as a signal generator, can be turned off.

(6) To preset the transmitter, place the set in the transmit position and adjust the transmitter tank adjustment screw for minimum plate current.

(7) Collapse the upper three sections of the antenna rod and connect the dummy antenna to the top of the rod. Connect the microphone to the M and G terminals of the junction box. Then adjust the dummy antenna capacitor control for minimum plate current. Whistle into the microphone and check the antenna current increase due to modulation as given in paragraph 73.

77. Replacement of parts.—a. Antenna rod.—(1) To replace the antenna rod, first the chassis must be removed from the case. The antenna rod fits into an insulated guide which is fastened to the chassis at the terminal board by a machine screw. The antenna rod


in the extended position is supported by a metal clamp attached to a polystyrene base. At the side of the clamp, where it is fastened to the polystyrene base, are three wiper contacts which grip the rod tightly. It is through these wiper contacts that the electrical contact to the antenna rod is made. An insulated plug in the bottom end of the antenna rod operates the toggle switch on the chassis.

(2) To remove the antenna rod, remove the screw which holds the antenna guide to the terminal board. Then gently bend the terminal board away from the antenna guide so that the plug at the end of the guide disengages from the hole in the terminal board. Exercise the areatest care in this operation as it is possible to tear the terminal board loose from its fastenings. Then with the guide unfastened, the antenna rod is withdrawn from the metal clamp.

(3) To replace the antenna rod, slip the antenna guide over the bottom section of the rod. Pass the antenna rod through the antenna guide ferrule and seat the ferrule at the top of the guide. Insert the tip of the antenna rod into the antenna clamp and push the rod through the clamp gently, until the top of the antenna guide comes in contact with the clamp. The antenna guide is then oriented so that the insulated end plug on the antenna rod will engage the lever on the power switch. Then very carefully bend the terminal board back slightly; just enough to permit the plug at the end of the guide to seat in the hole in the terminal board. Replace the fastening screw.

b. Replacement of resistor-capacitor cups.—(1) There are four resistor-capacitor containers which are called cups on the hottom of the chassis. These cups fit around the tube sockets and it will be necessary to unsolder the wires from the tube socket as well as the cup before removing. The cups are fastened to the tube sockets by cement and must be pried loose from the socket by a screw driver or a knife. The cup will be broken in the process.

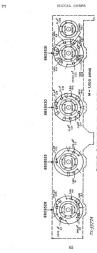(2) Each cup has a part number marked on it as well as a schematic drawing of the condenser and resistor connections. When replacing a cup, be sure that the new cup has the same part number as the old one. As a great number of wires will have to be unsoldered, it will be found helpful to put on paper a simple description of each wire removed and the point to which it connects. Reference to the cup diagrams shown in figure 23 also will be found helpful. The old cement should be scraped off the socket base before cementing the new cup in place. The new cups should be placed on the chassis so that the part number on the cup faces the back of the chassis, considering the press-to-talk switch side to be the front,





Caution: When soldering connections to a new cup be careful not to apply too much heat. The cup may be damaged beyond repair if this precaution is not observed.

c. To replace an i-f transformer—Disconnect the transformer wires, and remove the champs holding the transformer shield can to the chassis. Make a note of the transformer position so that the charge of the charge of the transformer position so that the originally were jotnevies, oscillation may result. The position of the transformer with respect to the trimmers in the top of the can should also be considered, so that the trimmers can be reached through the openings in the test heasing when alining the set. Make with the evieties, a condition which will result in a short circuit.



d. To remove an epicle—As most of the parts are fastened to the classis with epicks; removal of the epiclet is messary for the replacement of these parts. A simple and effective way to remove an epicle is to place a drill point of a diameter larger than the eyelet in a vise with the tip end up. Place another drill point of a similar diameter in a knew. Det the eyelet to be removed over the drill point in the vise, then apply the brace to the other side of the rivest and drill it out. Take acre to drill out only reough material to remove the rolled over edge of the eyelet. Do not drill through the classic. This will enlarge the hole and make the replacement of a new eyelet.


e. To replace pouser switch.—To replace the power switch it will be necessary to first remove the a-f choke and the two tubular capacitors next to the switch. Next remove the nut holding the switch to the chassis and then remove the wires to the switch. The switch now can be removed from the chassis by patient maneuver there.

- 78
- 78. Trouble location and remedy.—The following are possible troubles and their remedies
- a, Excessive r-f amplifier plate current in the transmit position,-(1) If the r-f amplifier grid excitation (the r-f voltage applied to the
- amplifier grid) is low, insufficient bias voltage will be developed across the grid resistor R., and the plate current will be excessive. Low grid excitation may be caused by a poor crystal or a weak or burned out oscillator tube. Also, no excitation would occur if the coupling capacitor C, were open or the oscillator were not functioning. See chart II for transmitter characteristics. (2) High plate current might be caused by an improper r-f am-
- plifier tank coil. An incorrect coil will show up in the inability to get a dip in the plate current reading of the r-f amplifier tube when tuning this stage.
- (3) High plate current could be caused also by short-circuited turns in the r-f amplifier coil. The effect would be the same as when using an incorrect coil. A leaky or short-circuited coupling capacitor

Chart II.—Chart of average transmitter performance characteristics											
Average	Minimum										
18 ms (r-f power: 18.1 mw).	15 ms (r-f power: 12.6 mw).										
20.5 ma (r-f power: 25.53 mw).	17.5 ms (r-f power: 17.0 mw)										
Over 50 percent	Over 50 percent.										
1.4 volts											
	Average 18 ms (r-f power: 18.1 mw), 20.5 ms (r-f power: 25.53 mw), Over 50 percent,										

C, would also cause excessive plate current.

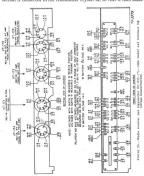b. Oscillator does not function (no reception and transmission).-To check for operation of the oscillator, place a d-c voltmeter across R.; a reading should be obtained if it is functioning. (See fig. 25 and chart III.) Besides the common reasons for oscillator inoperation such as part failure, a weak crystal, low battery voltages, etc., inoperation can also be caused by defective switching. If in pressing the press-totalk switch, the moving blade of switch section A does not make contact with the switch lug connected to the transmitter crystal M. at the same time or before the moving blade of switch section M shortcircuits resistor R₁₇₁ the energy pulse necessary to start crystal activity will not reach the crystal and the oscillator will not function. As a result of the high screen voltage and no bias, the tube VT-171 will become paralyzed. To remedy this trouble, move the lug on switch section 4 connected to the transmitter crystal M. se that it does make



contact at the same time or before switch section M short-circuits resistor R_{17} . Also replace the tube.

c. Audio oscillation in transmit position.—(1) If the r-f amplifier tube VT-174 becomes inoperative, the load offered to the modulator tube is removed. The plate load of the modulator tube then will be the impedance of the modulation choke, which is high. Under this condition, sufficient coupling exists between the input of the audio amplifier

and the output of the modulator to cause oscillation,

(2) Failure of the r-f amplifier tube VT-174 to operate can be caused by an open filament, gas in the tube, or loss of vacuum due to a crack in the glass. A cracked glass or gas in the tube will be indicated by a milky color near the exhaust tip of the tube.

d. Noise due to regeneration.—(1) A small amount of regeneration in the receiver is permissible, as it increases the selectivity and sensitivity of the receiver; however, because tubes of the same type vary somewhat in their gain characteristics, excessive regeneration may occur when tubes are changed in the receiver. Excessive regeneration results in a high circuit noise level, and in extreme cases causes oscillation. Recepteration is caused by coupling between circuit elements.

due to close spacing of parts on the chassis.

(3) The solution to this problem is to reduce the sensitivity of the receiver to a value which permits an allowable noise level. Provision for reducing the sensitivity of radio receiver and transmitter Re-Gill-(f) for ease of excessive repensariation is provided for by an Re-Gill-(b) for ease of excessive repensariation is provided for by an expensariation and the result of the result of

c. Sensitivity control adjustment—(1) If after the proper alinement of a receiver it is found that the sensitivity is greater than 7 microvolts for a 15-volt output reading on the 50-volt ac scale of the output meter, or 6 microvolts for a 20-volt reading on a vacuum-tube-volumeter type output meter, adjustment of the sensitivity control is recommended. This adjustment, however, should be made only after checking the receiver to see that the lack of sensitivity does not result.

from weak tubes, low battery voltage, or circuit failures. Charts IV and V give receiver performance figures.

(2) The sensitivity of the receiver is controlled by an adjustment of the grid bias on the r-f amplifier, mixer, and i-f amplifier tubes. The adjustable bias is obtained by means of the voltage divider made up of resistors R, R, and R25. To increase the sensitivity of the receiver, the bias should be reduced. The reduction in bias is accomplished by moving the wire connecting resistor R., to the voltage divider closer to the ground end of the divider. Minimum bias and greatest sensitivity will be obtained when this lead is connected to ground. Additional information on the sensitivity control is given in 78d (2).

f. Tube trouble.-(1) Tubes which have lost their vacuum because of a crack in the glass will usually have a milky color near the exhaust tip or base. The cracks are often plainly visible at the base of the tube.

(2) To avoid breaking tubes when removing them for inspection, remove the tube by inserting a rod through the metal tube in the center of the tube socket on the bottom of the chassis and by gently forcing the tube out. Be sure to remove the locking clip on top of the tube before forcing the tube out of its socket. g, Loose or tight adjustment of antenna trimmer,-A very loose or

very tight adjustment of the receiver antenna adjustment trimmer in

the receive position indicates an incorrect antenna coil. h. Loose connections.-(1) Some units may occasionally develop a

loose connection. This is the condition where a set becomes noisy when rapped gently. Loose connections most commonly occur when two metallic conductors momentarily break the contact they are expected to maintain. This may happen between the sections of the antenna rod, between batteries and their contacts, internally in tubes, or in some cases, a poorly soldered connection. (2) If a unit does develop a loose connection, the circuit elements at

fault may be located by gently tapping at various places on the unit with the insulated handle of a screw driver. The noise becomes louder as the loose connection is neared.

78

CHART III.-Point-to-point d-c voltage measurements

Component	Receiver	Trans- mitter	Volt- meter range	Сепреки	Receiver	Trans- mitter	Velt- meter range
R ₁	0	0	3	C11	NM	NM	
R ₄	0	0	3	C	50	90	300
R ₁	. 2	. 5	3	C11	0	75	300
R4	. 2	. 7	3	Cu	0	0	000
R	11	. 0	3	Cu	0	0	3
	15	90	200	Cu	0	0	1 3
R ₄	.2	0	3	C ₁₈	0	0	1 3
Rt		0	3	Cu	27	0	30
R	6	0	8		80	0	300
R	18	0	20	Cu	00	0	300
R ₁₀	18	0	30		0	0	
R ₁₁	28	0	30	Си	0	0	
R ₁₁		0	30	C _R	NM	NM	
Ru	0	0	3	Си	1.2	NM	
R ₁₄				Cu		NM	
	10	0	30	C4	NM		
	65	0	300	Си	. 2	. 2	1
	45	0	300	Сы	. 1	. 1	1 2
	15	15	30	Cw	NM	NM	
	18	0	30	R ₃₅	0.1	0	- 2
R ₁₀	0	0	3	R ₁₆	0	0	2
R ₁₁	65	60	300	R ₂₇	0	0	1 2
R#	. 5	5	30	C1	0	0	
R ₁₀	0	0	3	C1	- 5	80	300
R4	0	1	3	C1	24	80	300
C	NM	NM		Cnt	85	80	300
C	. 2	2	3	Cm	40	85	300
C	1	2	3	Cm	80	90	300
C	ŏ	ő	3	Cn	95	0	300
C	l ŏ	1. 3	3	1 La (La)	0	10	30
	NM	NM		- A4 (A4)		10	

All readings taken across component using the volt-chrimsteir of test set 1-56-(*). Readings shown we taken using a 1000 ohm/volt meter. No d-s voltmeter readings should be taken where the betters N appear in any column because of likely damage to the circuit. This is particularly true of d-c voltage

C_H voltage will depend on bias connection...
 La refers to SCR-586-A, and SCR-586-B. This component is marked L₄ in SCR-586-C.

CHART IV .- Average signal inputs for a fixed output (receiver)

1.	All values	taken with chards out of test case US-81-(*), RA-37 voltages 1.65 volts
		BA-37 voltage=1.65 volts, BA-38 voltage=190 volts,
4.	Receiver a	arphone, or equivalent, connected across receiver output.

grid.

Signal generator connected to—	Signal genera- tor frequency setting :	Dummy	Signal input to produce 29 volt output on V. T. V. ³	
Antenna	5205 ke	Through test stand FT-252-(*),	2.5 μV	3 av.
Antenna (image fre- quency),	6115 ke	Through test stand FT-252-(*).	1850 μV	2250 av.
Antenna	455 ke	.1 af	20,000 µV.	
R-f grid Converter grid	455 ke	.1 of	190 av	28 av.
Converter grid	455 ke	.1 µf	180 uv	180 av.
Microphone amplifier	1000 eps .	.1 pf	2400 µV	2400 µv.
grid. A-f output amplifier	1000 eps .	.1 µf	1.1 v	1.3 v.

1 Sizeal generator modulation—400 cm 200%.
3 Values linets in this column are for 20 voic output reading on a general radio type 720-A vacuum tube voiceater;
1 Values linets in this column are for 15-voic output reading on 20-voic a c range of selective analyzer of test

Chart V.—Average receiver performance characteristics

Test	Ave	rage	Minimum					
Test	Using V. T. V.	Using I-56-(*)	Using V. T. V.	Using I-56-(*)				
Sensitivity Image ratio Direct transmission ratio	3 µV 1 1 800 10,000	4 μv ^{2 4} 800 10,000	6 μv 11 200 4,000	7 μV ^{1 4} , 200. 4,000.				
Maximum audio out- put. A battery BA-37:	50 volts 1	22 volts 3	40 volts 1	18 volts.*				
Voltage Current B battery BA-38:	1.4 volts 235 ma		250 ms (max)	250 ms (max).				
Voltage Current	103 volts 11 ma	103 volts 11 ma	14 ma (max)	14 ma (max),				

Readings made on selective analyzer of test set 1-36-(*).
 20-volt output meter reading. Signal generator modulation 600 cps 3

SECTION V

SUPPLEMENTARY DATA

drwg, No.	-											-	-	
Mit.	•	3	€	•	€	0	3	€	_		€	€	3	
Panetica	Voltage blocking, Vi	Sereen grid bypass, Vi	Plate bypass, Vi	Grid neutralizing, V1	Grid bias bypass, V ₁	Oseillator feed-back	Receiver antenna tuning.	Filament bypass, V	Coupling, V, to V,, trans-	Coupling, V1 to V2, re-	Seroen grid bypass, Vr	Tuning, Is.	Ave filter	
Description	Fixed, paper, .006 M, ±20%, 100	Fixed, paper, .0005 µl, ±20%, 100 v, part No. 8A28549. Part	of N ₁ cup. Fixed, paper, .006 pd. ±20%. 100 v, part No. SB28528. Part	Fixed, ceramic, 7 and, ± 5%.	Fixed, paper, .006 pf. ± 20%. 100 v, part No. 8B28528. Part	Pixed, mica, 25 and, nominal, part	Variable, mica, 18-160 and, part	No. 20A2/459, Fixed, paper, .01 pd, ±20%, 100	Fixed, ocramic, 25 ant, ±10%.	Fixed, ceramic, 15 port, ±10%.	Type D, part No. 21A28817. Fixed, paper, .1 4f, ±20%, 100 v,	variable, air, 7-140 and, part No.	19A25090.	STATE OF STA
Name of part	Capacitor	ор	do	do	do	do	do	do	do	do	do	do	do	
Elgnal Corps stock No.	3DA6-41			3D9007-2		3D9025-36	3D9018V-4	3DA10-102	3D9025-35	3D9015-18	3DA100-120	3D9007V-1	3DA40-6	
Ref. No.	0	6	0	C.	Cc		G	C.	5	Chart	Charter	Carre	Carre	

				-								-		
	EE	€	€	0	33	8	0	€	€	0	€	3	0	£
Tuning, Le primary	Tuning, Ly secondary.	Plate bypass V ₁	Tuning, L, secondary	Detector bypass	A-f amplifier coupling	Grid bias bypass, V	Voltage blocking a-f out-	Plate bypass, V.	Sereen grid bypass, Vi	Coupling, Ve to Vs	Plate bypass, Vs	Screen grid bypass, Vs	Plate bypass, Vs	Plate bypass, V ₂
Variable, mica, 58 and, nominal, part No. 20A27340.	Pixed, paper, .01 µl. ± 20%, 100 v, part No. 8B28530. Part of	Fixed, paper, 51 of, ± 20%, 100 v. part No. 8B28530, Part of N.	Variable, mics, 28 unf, nominal,	Fixed, mice, 70-100 and, nominal,	± 20%, 100	Fixed, paper, .006 pd, ± 20%, 100	Fixed, paper, .02 pf, ± 20%, 100	Fixed, paper, .00025 af. ± 20%, 100 v, part No. 8B28531. Part	of N ₄ cup. Fixed, paper, .01 af, ± 20%, 100 v, part No. 8B28531. Part of	Fixed, paper, .006 µf, ±20%, 100 r, part No. 8B28531. Part of	Fixed, paper, .001 af, ±20%, 100	Fixed, paper, .075 pf. ±20%, 100	Fixed, paper, .13 of, ±20%, 100	Fixed, paper, .01 of, ± 20%, 100
do.	do	do	do	do	do.	do	do	do	-do	qo	-do	do	do	do
	3D9058V		3D9028V	3D9070-6	3D9007-1 3DA6-41	3DA6-42	3DA20-43				3DA1-85	3DA75-1	3DA150-2	
Call	30	Chr	С.	C	55	Cn	Ca	CB	ď.	J	Carrie	Car	Car	Co

Radio receiver and transmitter BC-611-(*)-Continued

						816	(NA)		one						
drwg, No.	24B29012	24B29012	24B29012	24B29012	24B29012	24B29012	24B29012	24B29012	24B29012	24B29012	24B29012	24B29012	24B29012	24B29012	24B29012
Mfr.	€	•	€	€	3	3	3	9	9	0	0	0	€	€	€.
Function	Antenna loading	do	-do	- op	do	do	do	- op	- op	do	-do	- op	do	-do	-do
Description	Antenna, range 3500-3675 ke (for	SCR-539-A). Antenna, range 3675-3825 ke (for	SCR-339-A). Antenna, range 3825-4025 ke (for	Antenna, range 4025-4225 ke (for	Antenna, range 4225-4425 ke (for	Antenna, range 4425-4625 ke (for	Antenna, range 4625-4825 ke (for	SCK-539-A). Antenna, range 4825-5075 ke (for	Antenna, range 5075-5300 ke (for	Antenna, range 5300-5500 ke (for	SCR-536-A). Antenna, range 5500-5775 ke (for	Antenna, range 5775-6000 ke (for	Antenna, frequency 4035 kc, part No. 24K34970 (for SCR-536-B	Antenna, frequency 4495 kg, part No. 24K34971 (for SCR-539-B	and C). Antonna, frequency 4930 kc, part No. 24K34972 (for SCR-536-B and C).
Name of part	Coll C-358	Coll C-359	Coll C-360	Coll C-361	Coll C-362	Coll C-363	Coll C-364	Coil C-365	Coil C-356	Coil C-367	Coll C-368	Coll C-369	Coll C-361	Coll C-363	Coll C-365
Ref. No. Etpnil Corps stock No.	3C299-358	3C299-359	3C299-350	3C299-361	3C299-362	3C299-363	3C299-364	3C299-365	3C299-366	30299-367	3C299-368	3C299-369	3C259-361	30299-363	3C299-365
Ref. No.	L	L,	L1	L	L	L	L	L	L	L	L	L1	I	I	7

Coil C-366
Antenna, frequency 5500 kc, part No. 24K34975 (for SCR-536-B
R-f tank, range 3500-3825 ke (for
R-f tank, range
R-f tank, frequency 4035 ke, part No. 24B35222 (for SCR-536-B
R-f tank, frequency 4495 ke, part No. 24K35223 (for SCR-536-B
R-f tank, freep
R-f tank, frequency 5205 ke, part No. 24K35225 (for SCR-556-B
R-f tank, frequency bart No. 24K35226
R-f tank, frequency 5500 kc, part No. 24K35227 (for SCR-536-B

Ref. No.	Signal Corps stock No.	Name of part	Description	Purction	Mffr.	Oalvin drwg. No.
	3C362-17	Codl	R-f choke; .5 mb, part No.	Oscillator, V ₂	€	
C. CLO	2C5351A/A4	do	I-f input transformer and shield,	Coupling Vr-Va	€	
C, (L ₀)	2C5351A/A5	do	I-f output transformer and shield,	Coupling, Vy-V4	3	
4 (L ₄)	3C362-16	do	Audio output reactor; 590-850 ohms d-c resistance, part No.	Output plate load	€	
J	2Z3543.50	Crystal	25A28551. Receiver crystal (Specify fre-	Receiver stability con-	3	48B27212
	2Z3543.50	-do	part No	Transmitter frequency	Ė	48B27212
· · · · · ·	3Z8318.	Switch	Change-over switch, eight-pole,	control. Send-receive.	€	
	2C5351A/A3	Merophone	double throw, part No. 40B25825. Microphone and leads assembly,	Transmission	3	
	2C5351A/A3	- op	Agnormac, part No. 1331038. Microphone and leads assembly, crystal (Early issue of SCR-	op	€	
,	2C5351A/A2	Earphone	pus	Receiving	3	
	2C5351A/A2	op	dynamic, part No. 1X31094. Earphone and leads assembly, erystal (Early issue of SCR-	-do	3	
-	3Z9853	Switch	536-A). Toggle, DPST, part No. 40A25820.	Filament and plate power	0	
f	3.438	Battery	103.5 volts, Type BA-38, B, part	supply. Plate power supply		
	3A37	do	115, volt, Type BA-37-A, part	Filament power supply		
	2Z11100.1 2Z11100.1	Tube shielddo.	Metal shield, part No. 26A27204	VT-174 shield	EES	

Manual and the state of the sta
Authoris, Capacidor ensisted Capacidor ensistente Capacidor ensistente Capacidor en entre en entre en entre en entre e
Authernative Capacitor-resistor Capacitor-resistor-r

Bef. No. 9	Signal Coeps stock No.	Name of part	Description	Punctica	Mfte.	drwg, No.
	3Z804A7-Z	Resistor	Fixed, carbon, 4.7 megohm, ± 10%, % watt, not insulated,	Ave filter.	€	
Кв	3Z6647-5	do	Fixed, carbon, 47,000 ohms, ± 10%, % watt, insulated, type	Plate dropping, V1	*	
К	3Z6633-3	do	MB ½ INS, part No. 6B6323. Fixed, carbon, 33,000 ohms, ± 10%, ½ watt, insulated, type	Plate dropping, V ₄	4	
		dodo	MB ½ INS, part No. 6B6448. Fixed. carbon, 68,000 ohms, ± 10%, ⅓ wart, not insulated, part No. 8B28530. Part of N;	Serveta grid dropping Vs	€	
	326722-4	do	Fixed, carbon, 220,000 ohms, ± 10%, % watt, not insulated.	Detector filter, V.	00	
		do	type 997-A, part No. 6B5571. Fixed, carbon, 1 megohm, ± 10% % watt, not insulated, part No.	Detoctor load, V4	€	
		do	SBZSS31. Part of N. cup. Fixed. carbon, 6.800 ohms, ± 10%, 5 watt, not insulated, part No. SBZSS30. Part of N.	Plate dropping, Va	0	
	3Z6733-2	- qo	Fixed, carbon, 330,000 ohms, ±	Serotn grid dropping, Vs	**	
	3Z6627-7	do	MB ½ INS, part No. 8B6356. Fixed, carbon, 22,000 ohms, 4 10%, ½ wats, insulated, type	Sereen grid dropping, V ₂	4	
Rai	326722-9	do	MB ½ INS, part No. 6B6370. Fixed, earbon, 229,000 ohms, ± 10%, ½ watt, insulated, type MB ½ INS, part No. 6B63464	Seroen grid dropping, V1	4	

2000 0-4,		04	V ₆ (*)	(*)	,	h 6 4	+	01	, , , , , , , , , , , , , , , , , , ,	alk (*)	(e)	(•)	T- (*)
2000 2,	Plate dropping, Va	Grid Bias, Ve	Serven grid dropping, Ve	Plate load, V.	Grid blas, Vs	Server grid decoupling, V ₂ ,	Sensitivity control	Ave filter	Damping	Part of push-to-talk	dododo	Cover for antenna	Holds VT-172 and VT- 174 in socket,
In 2000% A A		Fixed, carbon, 10 megohm, ± 10%, ½ watt, insulated, type	Fixed, carbon, 3.3 megohm, ± 10%, ½ watt, not insulated, part No. 8B28531. Part of N.	Fixed, earbon, I megohm, ± 10%, kwatt, not insulated, part No.	Fixed, carbon, 3.3 megohm, ± 10%, ½, watt, insulated, type	Fixed, carbon, 3,900 ohms, ± 10%, ½ watt, irenlated, type	MB ½ 1NS, part No. 985973. Fixed, carbon, 6,800 ohms, ± 10%, ½ watt, insulated, type	MB ½ INS, part No. 6B6350. Fixed, earbon, 4.7 megohm, ± 10%, ½ watt, insulated, type	EB INS, part No. 6B6391. Fixed, carbon, 470,000 ohms, ± 10%, % watt. insulated, type	Metal, 2" long, 96" wide, part No.	Metal, 13% long, %s" wide, part	Aluminum cap, 1%," diameter, 3%, high, beaded chain 4"	Abuminum, W" x W", Ne" bole with rubber groumet, part No. 1X30139.
220810-6			do	do	do	do.	do	do	do	Arm, switch lever	Arm, switch lever	Assembly, antenna cap and chain.	Assembly, bracket and grommet.
	326768-3	R ₂₁ 3Z6810-6			Rm 3Z6803A3-1	3Z6390	R ₁₅ 3Z6568-9	- 1	Rg. 326747-6.	3Z8318/L1	3Z8318/L2	28536A/A1	2C5351A/A6

P	
tinne	
ŝ	
0	
19-08	
itter I	
ransm	
and t	
eceizer	
Radio rece	
P	

f. No. 1	f. No. 1 Eignal Corps stock No.	Name of part	Description	Punction	Mite.	Oabrin drwg, No.
0	28636A/A3	Assembly, bottom cover.	Metal, 3½," x 3½", complete with battery contactor plate and	Bottom cover of housing and battery contactor.	€	
d	2C536A/A3/3	Assembly, and plate.	springs, part No. 1X28692, Bakelite, 3½" x 1½" complete with terminals and contacts	End plate of chassis	€	
2	2C336A/A3/4	Assembly, filler and clips.	part No. 1X28667. Fiber, 1¼" wide, 11¼" long, elip riveted on each end, part No.	Used to fill space between battery BA-38 and	€	
	28536A/A3/1	Assembly, spade bolt and cover.	1X29056. %" spade bolt with %" diameter, knurled edge nut, part No.	housing. Holds bottom cover shut.	3	
4	28536A/A2	Assembly, strap	Olive drab strap, 114" wide, 30"	Carrying strap	9	
6	28536A/A4	Assembly, top cover.	dong part No. 1.A.20091. Aluminum, 3¼" x 3¼" complete with battery spacer and springs, antenna insulator, moisture scal and strap hanger, part No.	Top cover of housing	€	
6	2A292-2/3	Ball end, antenna.	IX28688. Marblette ball, 37" diameter, olivo	On tip of antenna to aid		
7	2C5351A/J2/2	Bezel, data plate	drab finish, part No. 67A27209. Aluminum frame 2%" x 36", part	Frame for data plate	0	
	3Z8318/B1	Bracket, switch	Metal 34" x 54", with a .144"	Part of push-to-talk	3	
	2Z11100.1/1	Bracket, tybe re- tainer.	Aluminum, 3," x 3," with 31s," hole, part No. 7A25088.	Holds tube shield for VT-174, VT-171, and	①	
0	2C5351A/A2/1	Cap, phone, and	Molded bakelite, 25," diameter,	Cap for mouthpiece and	0	
1	222626.3	Clamp, capacitor	Brass, semicircular, 16" radius, nart No. 42.428454.	Holds capacitor Cp	3	

	27,2645	Clamp, erystal	Phosphor bronze % wide L	AVOID ULY STANS		
113	2C5351A/J2/1	Cover, data plate	Clear vinylite, 15" x 156", part	Transparent cover for	£	
114	2Z3401.1	Cover r-f ehoke	No. 61 A28450. Bakelite, 1" long, 3" outside dlam-	Cover for r-f choke Lq	€	
115	3Z8318/C2	Cover, switch	Acetate celluloid, 114" x 1014",	Cover for change-over	3	1
116	3Z8318/C1	Cover, switch	Molded rubber, 13" x 4", part		€	
711	3ZS318/F1	ver	Aluminum frame 13," x 4" with 6 holes .156" diameter for-		€	
118	3Z8318/M1	Fulerum, hinge	mounting, part No. 42B25987. Alcos metal, one .156" hole for mounting .067" hole for hinge	Part of push-to-talk switch assembly.	€	
119	2.A292-2/4	Guide, antenna	Molded 75/6" long, 282" diam-	Guide for antenna	€	i
120	2C5351A/J2.1	Housing	Housing, less all parts, 115, x 3"	Housing for unit	€	
121	3Z8318/L3	Link, sliding hinge.	Metal, 1%" x %6", slotted, hole at-	Part of push-to-talk switch assembly.	€	
122	No number to be	Nameplate	Vinylite, 15" x 35", black back-	Model, order and serial	€	13B2854
123	2C5351A/N1	Nut, chamfered	Brass, nickel plated, Ne-23 x Ne",	Tank capacitor mounting.	€	İ
124	285351A/A3/2	Pin, groove	W. long, .093", diameter, metal,	Hinge pin for mounting	€	1
125	3Z8318/P1	Pin, hinge	W long, 0.125" diameter, 4-36 thread on one end, part No.	Part of push-to-talk switch; holds long and	Ť	
126	3Z8318/P2	do	0.672" long x 0.062" diameter,	short levers together. Part of push-to-talk	Ť	-
127	2C5351A/J2/4	Plate, data	Vinylite plate, 15," x 15," part No. 13A28455.	Frequency, channel and battery date informa- tion plate.	T	

79

72
ž
.5
ä
-6
Y
н
•
٣
÷
3
9
30-61
BC-61
er BC-61
itter BC-61
mitter BC-61
nsmitter BC-61
ransmitter BC-61
transmitter BC-61
vd transmitter BC-61
and transmitter BC-61
r and transmitte
ver and transmitter BC-61
r and transmitte
r and transmitte
ceiver and transmitte
ceiver and transmitte
adio receiver and transmitte
o receiver and transmitte

Bet. No.	nation code were var-	Name of part	Description	Punction	Mffr.	drug. No.	
28	2C3351A/S1	Plug, jumper	Molded bakelite over wire jumper, %4" x W", part No. 28A28535.	Jumper for plate meter terminals when meter			
129	28586A/A2/3	Rod, housing and strap, support	 long, ½," diameter, threaded at one end, part No. 46K27220. 	is not used. Bottom cover hinge rod and strap support.			
	28586A/A2/2	Rod, housing and strap, support	1½" long, ½g" diameter, threaded at one end, part No. 46A25849.	Top cover hinge red and strap hanger support.			
131	28536A/A4/1	Seal, moisture	Rubber, %" diameter, %" hole, part No. 37A27308.	Weatherproofing at an- tenna through top			-
32	28536A/A3/5	Seal, rubber ring.	Sponge rubber ring, 14", 3%," x.	tom c			
33	2ZS761-10	Soeket, erystal	2-crystal receptacle, part No.	Socket for two erystals	€		_
134	2C5351A/81	Spring, coll re- tainer.	Phosphor bronze, ¾" x ¼" with .127" diameter hole for mount-	Tank coil retainer spring.	€		
	328318/82	Spring, cushion	ing, part No. 41A25995. Phosphor bronze, W" x W" spring,	Part of push-to-talk	3		
	3Z8318/81	Spring, switch lever.	part No. 41A28452. Stainless steel spring, part No. 41A27203.	switch assembly. Lever return spring, part of push-to-talk switch	€		
	228669-6	Tube socket	7 prong ministure	Assembly, VT-171, VT-172, VT-	9	946794	
138	228669-6	do	6 prong ministure, part No. 9K6796.	173, tube socket. VT-174 tube socket.	€	946794	

SIGNAL CORPS

80. Names and addresses of manufacturers.

Mig. No.	Name	Street address	City	State
1	Centralab	900 E. Keefe Ave.	Milwaukee	Wisconsin.
2	Allen Bradley Co		Milwaukee	Wisconsin.
3	Carborundum Corp	Globar Divi- sion.	Niagara Falls	New York.
4	Stackpole Carbon Co	Elk County	St. Mary's	Pennsylvania

INDEX	Paragraphs	Denn
Adjustments:	Langrapus	rage
Alinement	62.74	40.5
Presetting	72, 73	33, 36, 50, 51
Antenna coil:		
Replacement	55, 70	29, 44
Tuning	58, 72	33, 50
Batteries:		
Installation	11	
Life.,	4	- 2
Testing	63	40
Type used	4	
Bias, adjustment	78	64
Change of frequency	54, 69	28, 43
Change-over switch:		
Adjustment	78	64
Functioning	37	18
Coils:		
Frequency range of (chart I)	70	44
Replacement	55, 70	29, 44
Components:		
Description	9	
Weights and dimensions	2	
Controls;		
Location	8	5
Operation	13, 16	7. 5
Power switch	13	7
Push-to-talk switch.	15	8
Crystal activity test.	57	33
Crystal earphone	9	- 7
Crystal microphone	9	. 7
Prystals; replacement of	55, 70	29, 44
Receiving	58	35
Transmission	59	36
Description of components	9	- 1
Difference between SCR-536-A, B, and C.	1	- 5
Dimensions of components	2	- 3
Distance range	5	4
Carphone:		
Crystal	9	5
Inductor.	9	5
Employment	10	6
requency coverage	6	4
		90 19
requency presetting		

INDEX

I-f amplifier:	Paragr	phs Pages
Alinement	62.74	40.54
Functioning		40, 54
	28	14
Input power		
Locating trouble 23, 4	7, 48, 78	10, 23, 64
Manufacturers' addresses	. 80	81
Measurements, voltage (chart III).		
Microphone-		
Amplifier, circuit		17
Crystal		5
Inductor	. 9	5
Modes of transmission and reception	. 7	5
Modulation:		
Percentage	. 59, 73	36, 51
Circuit	. 36	17
Netting	. 18	9
Operation	. 13	7
Oscillator, eireuit	. 33	17
Parts:		
List of replaceable	79	70
Replacement 5		29, 44, 60
Poor reception and transmission		10. 23
Power amplifier:		10, 20
Circuit	34	17
Tuning		33, 51
Preparation for use		7
Presetting receiver with IE-15-A		50
Presetting receiver with IE-13-A.		33
Presetting receiver with IE-15-A.		
Presetting transmitter with IE-15-A. Presetting transmitter with IE-17-(*)		51
		36
Procedure in locating trouble		10, 23, 64
Rain, operation in	. 22	10
Receiver:		
Alinement	62, 74	40, 54
Characteristics (chart V). Functioning		
	. 24	11
Presetting 55-58		29, 43
Sensitivity		.64
Receiving		8
Removal of eyelet	. 77	60
Repairs	77, 78	22, 60, 64
Replacement of—		
Antenna coil	55, 70	29, 44
Batteries.	- 11	6
Crystals	55, 70	29, 44
Earphone		23
I-f transformer		60
Migrophone		23
Power switch		60
R-f tank coil	55, 70	29, 44

INDEX

	Paragray	phs Page
Setting up test equipment IE-15-A	71	4
Setting up test equipment IE-17-(*)	56	3
Starting set.	13	
Switch, change-over:		
Adjustment	78	6
Function.	37	1
Operation	15	
Test case CS-81-(*)	64.65	24. 4
Test equipment IE-15-A	64	4
Test equipment IE-15-A, presetting with	69	- 4
Test equipment IE-17-(*)	50	2
Test equipment IE-17-(*), presetting with	54	2
Test harness'	67	4
Test set I-56-(*)	68	4
Test stand FT-252-(*) 50, 52	64 66	24. 4
Test unit I-135-(*) 50, 53, 56	69 69	24
(,,,,,,,,,,,,,,,,,,,,,,,,,,,		25, 32, 4
Testing batteries	63	40, 02, 4
Total weight	3	- 1
Transmitter:	0	
Characteristics (chart II)	78	6
Circuit		1
Presetting 55, 56, 57, 59, 70	71 70	29
		32, 33, 30
		44, 45, 5
Transmitting	15	22, 20, 0
Trouble, location 23, 47.	10 70	10, 23, 6
Tubes, vacuum:	40, 10	10, 24, 6
Base connections (fig. 24)		0
Replacement	77 41	2
Vacuum tube base connections (fig. 24)	77	6
Vacuum tubes, replacement of		
Voltage measurements (fig. 25 and chart III)	41	2
Weak signals, cause of	78	6
Weights:	47	23
Components.		
	2	
Total	3	
[A. G. 002.11 (1-29-43).]		
BY ORDER OF THE SECRETARY OF WAR:		
G. C. MARS	SHALI	4
	hief of	
J. A. ULIO		

Major General, The Adjutant General. DISTRIBUTION:

B 5 (2); R 7 (3); Bn 7 (5); I Bn 5, 44 (5); I C 5 (10), 4, 7, 44, (5) and 11 (4).

(For explanation of symbols see FM 21–6.) $\,\,$ 84

TECHNICAL MANUAL

RADIO SETS SCR-536-A, SCR-536-B, SCR-536-C, AND SCR-536-D

CHANGES | WAR DEPARTMENT.

No. 1 Washington 25, D. C., 15 December 1943.

TM 11-235, 14 May 1943, is changed as follows: The title of this manual is changed to read "RADIO SETS SCR-

The title of this manual is changed to read "RADIO SETS SCI 536-A, SCR-536-B, SCR-536-C, and SCR-536-D." [A, G, 305.7 (20 Nov 48).] (C1, 16 Dec 48.)

1. Use.

"Badio sets SCR-539-A, SCR-539-A, SCR-539-C, and SCR-539-D are allike for all practical purposes. The different suffix " * exists between types. Similarly the component parts, radio receivers and transmitters BC-611-A, BC-611-B, BC-611-C, and BC-611-D are referred to as radio receiver and transmitter BC-611-C). Test equipments IE-17-A, IE-17-B, IE-17-C, are referred to as In-17-B, IE-17-B, IE-17-

[A. G. 309.7 (20 Nov 43).] (C 1, 15 Dec 43.)

		- 3	Dimen	sioess (i	neber)	1	=
Quantity	Article	Height	Width	Depth	Length	Diameter	Unit weigh
1	Tube set GK-174 (spare): Consisting of: 1 tube VT-171—1R5 1 tube VT-172—185 1 tube VT-173—1T4 2 tube VT-174—384						.0
1	Box BX-49 containing: 1						
1	12 sets of r-f tank coils. (1 set of coils and operating frequencies.) Microphone cover M-367						

^{*} Commonent of SCR-535-D only

[[]A. G. 300.7 (20 Nov 43).] (C 1, 15 Dec 43.)

[[]A. G. 3007 (20 Nov 43).] (C 1, 15 Dec 63.)

*The individual items in this change will be cut apart and pasted over the specific paragraphs

or subparagraphs affected.

- 22.1. (Added.) Operation in freezing weather and dust.—
 a. When the set is used in freezing weather, moisture from the breath
- a. When the set is used in freezing weather, moisture from the breath condenses and freezes, plugging the holes in the microphone cap and making transmission impossible. This freezing condition can be prevented by the use of microphone cover M-367 which also serves as protection against sand or due.
- b. The cover is made of a light, water-repellent fabric with a drawstring or elastic band for holding it tightly over the microphone on the set. The cover is not waterproof and will not protect against
 - immersion in water or against long exposure to tropical humidity.

 c. Microphone cover M-367 will be used whenever the radio set is operated under freezing, dusty, or sandy conditions.
- d. All organizations will requisition one microphone cover M-367, stock No. 2B1567, for each radio set SCR-536-(*) on hand, if the set is not already provided with the cover. OCSigO Supply Letter No. 173, 10 August 1943, authorizes this requisition.
 - e. New issues of radio sets SCR-536-(*) will be supplied with the cover as a component part.
 - [A. G. 300.7 (20 Nov 43).] (C 1, 15 Dec 43.)

Oscillator.


a. (Added.) In radio receiver and transmitter BC-611-D and late models of BC-611-C, resistor R₂s is added in series with the screen circuit of V₂ (VT-171). R₂s reduces the screen voltage in the transmit position to eliminate the possibility of oscillator failure when using a tube VT-171 having low emission.

[A. G. 300.7 (20 Nov 43).] (C 1, 15 Dec 48.)

Change-over switch.

l. Sections L and * * * * L and M. In radio receiver and transmitter BC-611-D and late models of BC-611-C, resistor $R_{\rm rs}$ is placed in series with the screen of $V_{\rm 2}$ in the transmit position.

[A. G. 300.7 (20 Nov 48).] (C 1, 15 Dec 43.)

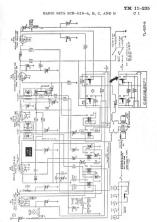

POURS 17.—Radio receiver and transmitter BC-611-B, BC-614-C, and BC-411-B—schematic diagram.

[A. G. 300.7 (20 Nov 43).] (C 1, 15 Dec 43.)

TM 11-235

RADIO SETS SCB-536-A, B, C, AND D

78. Trouble location and remedy.

CHART IL-Chart of average transmitter performance characteristics

T	est		Average			Misimon	4
R-f curren Unmodu Modula	lated	18 ma (r-f 20.5 ma (r mw).	power: r-f powe	181 mw). r: 255.3	15 ma (r-f 17.5 ma mw).	power (r-f)	126 mw) power: 170

CHART III -Point-to-point d-c voltage measurements R₁₇-----(5) 10 . 1

* Refers to SCR-536-D and late models of SCR-536-C. [A. G. 300.7 (20 Nov 43).] (C 1, 15 Dec 43.)

79. Table of replaceable parts.-Radio receiver and transmitter BC-611-(*).

R	ef.	Signal Corps stock No.	Name of part	Description	Function	Mfr.	Galvin drwg. No.
-							
1	Rg						
i	R ₂₈	3Z6470-9	Resistor	Fixed carbon, 4,700 ohms, 10%, 1/3 watt, insu- lated, type MB1/3 INS, part No. 6B6351.	Screen grid drop- ping, V ₂ .	4	
11	13						
	31/2	2B1567	Cover, micro- phone.	Light, water- repellent fabric with drawstring or elastic band.	Protect micro- phone.		
							*

BY ORDER OF THE SECRETARY OF WAR:

OFFICIAL: J. A. ULIO.

Major General,

The Adjutant General.

G. C. MARSHALL, Chief of Staff.

SUPPLEMENT 1 JULY, 1944 TM 11-235

SUPPLEMENT to

TECHNICAL MANUAL

RADIO SETS SCR-536-A, SCR-536-B, SCR-536-C, SCR-536-D, and SCR-536-E

The following information, published on Orders No. 10756-Phila-44-01 and 16090-Phila-44-01, supplements TM 11-255, 14 May 1943, and Changes No. 1, 15 December 1943. Personnel using the equipment and having custody of this technical manual will attach this supplement securely inside the front cover of the TM, and will enter suitable notations beside each changed paragraph and figure in the TM to indicate the presence of this supplementary information.

- Page 2, Par. 1. As modified by Changes No. 1, the last sentence should read: Test equipments IE-17-A and IE-17-E are referred to as IE-17-(*).
- Page 5, Par. 9σ. Add the following: In radio sets SCR-536-() beginning with serial No. 14,800, the paper cones have been changed to bakelite to improve sensitivity and resistance to moisture.
- Page 5, Par. 9b. Add the following: In radio sets SCR-536-() beginning with serial No. 14,800, the switch mechanism has been re-designed, and the component parts have been made of steel stampings to minimize breakage. The complete switch is interchangeable, but the component parts of these two switch assemblies are not interchangeable.

This Supplement also applies to Order No. 26828-Phila-44-01.

54P55717—Issue O

- Page 5, Par. 9c. Add the following: The bottom cover has been redesigned to fit better when closed. The moisture ring seal has been increased in thickness. This provides better moisture exclusion.
- Page 5, Par. 9s. Add the following: The moisture ring seal in the top cover has been increased in thichease. This insuras a better closing fit for the cover and provides better moisture exclusion. The antenna insulator assembly in the top cover has seal to a polystyrene miterial with a roll-on netal cap of soft brass, containing a viville gasket for moisture exclusion. This results in improved rf performance due to lower loses: in the polystyrene, and better moisture in cellulor loses. In the polystyrene, and better moisture exclusion
- Page 6, Par. 9f. Add the following: An antenna support of polystyrene has been incorporated in the set near the antenna end of the chassis to act as a support for the antenna rod and to prevent breakage of the antenna guide during servicing or in case of rough handling.
 - Page 19, Par. 38a. Add the following: The capacitor-resistor containers have been re-designed, using solder lugs throughout.
- Page 21, Par. 38e. Add the following sub-paragraph after sub-paragraph (2): (3) The i-f output transformer has been re-designed to increase the over-all sensitivity of the set.
- Page 69. In the table of contents under section V, insert the following title after paragraph 79:
 Maintenance parts list for radio set SCR-536-A. SCR-
- 536-B, SCR-536-C, SCR-536-D, and SCR-536-E... 79.1
 Page 70, Par. 79. Add the following notice under the heading Table of replaceable parts.—Radio receiver and transmitter BC-611.*

NOTE: See paragraph 79.1 for supersession notice.

Page, 80. Add the following paragraph after paragraph 79:

79.1 Maintenance parts list for radio set SCR-536-A, SCR-536-B, SCR-536-C, SCR-536-D, and SCR-536-E.

NOTE: The following information supersedes paragraph 79 for purpose of requisition.

NOTE: Failure or unsatisfactory performance of equipment will be reported on W.D., A.G.O. Form No. 468. If this form is not available see TM 38-259.

79.1 Maintenance Parts List for RADIO SETS SCR-536-A, SCR-536-B, SCR-536-C, and SCR-536-D. NOTE: Order maintenance parts by stock number, name and description.

			Distant	bear Bun-					
Ref.	Signal Corps	Name of part and description	Per	per ning Orga unit spares stock	Orgn	3d ech	4th ech	5th ech	Depot
	150	CAPACITOR: fixed; paper; 0.006 µf = 10%; 100 v dc (working).	1						•
3	3D9007-2	CAPACITOR: fixed; orramic; 7 µf =5%; 500 v; temp. coef.	1				•	•	•
Ca. Cr	3D6205-36	CAPACITOR: variable; fixed section 25-suf, variable section 18-to 160-puf; ceramic base.	1				•	•	•
	3DA10-102	CAPACITOR: fixed; paper; 0.01-µf = 20%; 100 v dc (working).	1			•	•	•	•
3	3D9025-35	CAPACITOR: fixed; ceramic; 25-usf #10%; 300 v; temp. coef. 0.00075-usf #15%.	1			•	•	•	•
C10	3D9015-18	CAPACITOR: fixed; ceramise; 15-pat #5%; 500 v; temp. coef. 0.00075-pat #15%.	-			•	•	•	•
Cit	3DA100-120	CAPACITOR: fixed; paper; 0.1-µf ±20%; 100 v dc (working).	-			•	•	•	•
S. C.	3D5007V-1	CAPACITOR: variable; air; 7- to 135-µ4f; coramic base.	1				•	•	•
Cos	3DA6-41	Same as C1.	1			•	•		•
Case	3DA20-43	CAPACITOR: fixed; paper; 0.02, pl = 10%; 100 v dc (working).	-			•	•	•	•
:	3DA1-85	CAPACITOR: fixed; paper; 0.001-µf =10%; 100 v dc (working).	1					•	•

aintenance Parts List for RADIO SPTS SCD 824 A SCD 524 D COD 524 C

	Signal Corps stock No.	Name of part and description	Ouan.	Ouan. Run- per ning	Orga	34	44	Sth	Depot
Czs 3	3DA75-1	CAPACITOR: fixed; paper; 0.075-uf = 20%; 100 v dc (working).							
C30 3	3DA130-2	CAPACITOR: fixed; paper; 0.13-µf = 20%; 100 v dc (working).	-				•		
2 17	30299-358	COIL C.338: antenna; range 3,500-3,675 lc; (for SCR-536-A).	-						
.1 5	3C299-359	COIL C.339; antenna; range 3,675-3,825 lc; (for SCR-536-A).	-						
.1 .5	3C259-360	COIL C-360; antenna; range 3,825-4,025 loc; (for SCR-536-A).	-						
	3C299-361	COIL C-361: antenna; range 4,025-4,225 kc; (for SCR-536-A).	-						
6	3C299-362	COIL C-362: antenna; range 4,225-4,425 kc; (for SCR-536-A).	-						
3	3C299-363	COIL C-363: antenna; range 4,425-4,625 kc; (for SCR-536-A).	1						
.1 3	3C299-364	COIL C-364: antenna; range 4,625-4,825 kc; (for SCR-536-A).	1			•			
.1 3	3C299-355	COIL C-365: antenna; range 4,825-5,075 kc; (for SCR-536-A).	1				•		
3	3C259-366	COIL C-366; antenna; range 5,075-5,300 kc; (for SCR-536-A).	1						
60	3C299-367	COIL C-367: antenna; range 5,300-5,500 kc; (for SCR-539-A).	1				•		
. 3	3C299-368	COIL C-368: antenna; range 5,300-5,775 kc; (for SCR-536-A).	1				•		
71 3	3C299-389	COII. C-369: antenna; range 5,775-6,000 kc; (for SCR-536-A).	-						
L2 38	3C259-370	COIL C-370: antenna; range 3,500-3,825 kc; (for SCR-536-A).	-			•			

				٠			•		•	•
							•		•	
					•		•F152000000000000000000000000000000000000		•	
										•
1	1	-	1	-	1	1	18 E	-	-	* 1
COIL C-371: r-f tank; range 3,825-4,225 kc; (for SCR-636-A).	COIL C-372: r-f tank; range 4,225-4,625 kc; (for SCR-E36-A).	COIL, C-373: r-f tank; range 4,625-5,075 kc; (for SCR-536-A).	COIL C-374: r-f tank; range 5,075-5,500 kc; (for SCR-535-A).	COIL C-375: r-f tank; range 5,500-6,000 kc; (for SCR-536-A).	COIL: r-f choke; (0.5 mh).	COIL: n-f (590-850 ohms d-c resistance; potted in can).	CANNA MAI DILEMENT AND PRODUCE AND PRODUCE AND	SWITCH: change-over; (single-pole, double-throw).	MICROPHONE ASSEMBLY: dynamic; (permoflux; with leads and rubber grommet).	EARPHONE ASSEMBLY: dynamic; (permoflux; with leads and rubber grommet).
30299-371	3C299-372	30299-373	3C259-374	3C1084B-5	9C362-9	3C362-16		328318	281709	2B475
La	Li	Li	La	Lz	Ls	Li	M,	Ms	M.	Ms

**

Ref.	Signal Corps stock No.	Name of part and description	Ouan. per unit	Ouan, Run- per ning unit spares	Run- ning Orgn spares stock	b de	44	Sth Depo	Depo
Me	323653	SWITCH: toggle; double-pole, single-throw; (for SCR-538- CZE); (for SCR 536-A, B, C).	-						
Mr	3A38	BATTERY BA-38-B; 103.5 v.	1					•	
Ms	3A37	BATTERY BA-37-A: 1.5 v.	1						
Ms	2211100.1	SHIELD: tube; cylindrical aluminum.	es				•		
Mis	2A292-2	ANTENNA: (telescopic; 4 section).	1					•	
Mis	2A292.2/3	BALL END: antenna; marblette ball; (for SCR-536-A.B.C).	1						
R2	3RC20AE105K	RESISTOR: fixed; carbon; 1 msg *10%; ½-w; (for SCR-536-A.B.C.).	1			•	•	•	•
Rs	3RC10AE105M	RESISTOR: fixed; carbon: 1 meg *20%; ¼-w; (for SCR-536-CZE).	1			•	•	•	•
Rs	3RC10AE332K	RESISTOR: fixed; carbon; 3.300 ohms = 10%; 14-w.	1					•	
Re	3RC20AE474K	RESISTOR: fixed; carbon; 470,000 ohms \$10%; 34.w; (for SCR-536-A.B.C).	69			•	•	•	•
82, R28	R7, R18 3RC10AE472K	RESISTOR: fixed; carbon; 4,700 ohms = 10%; 34.w.	63			•	•	•	
R10	3RC10AE473K	RESISTOR: fixed; carbon; 47,000 ohms #10%; 34-w.	1				•		•
Rit	3RC10AEXSK	RESISTOR: fixed: carbon: 33,000 obms +10%: 14.w							•

	•		•		٠	٠							•	•	
•	•		•		•		•	•					•		•
•	•				٠	•		•	•	•			•	•	•
•	•	•	•	•	•	•	٠	•							
-															
1	-	-	-	-	-	-	-	-	1	-	-	-	-	-	-
RESISTOR: fixed; carbon; 330,000 ohms +10%; ½-w.	RESISTOR: fixed; carbon; 22,000 ohms = 10%; 1/4-w.	RESISTOR: fixed; carbon; 220,000 ohms +10%; ½-w.	RESISTOR: fixed; carbon; 680,000 ohms +10%; ¼-w; (for SCR-536-A,B,C).	RESISTOR: fixed; carbon; 10 meg =10%; ½-w.	RESISTOR: fixed; carbon; 3.3 meg = 10%; 1/4-w; (for SCR-536-A.B.C).	RESISTOR: fixed; carbon; 3.900 ohms =10%; ¼-w.	RESISTOR: fixed; carbon; 6,800 ohms = 10%; 1/4-w.	RESISTOR: fund; carbon; 4.7 meg =10%; ½-w; tlor SCR. 556-A.B.C).	TRANSPORMER: 1-f input; 455 kc.	TRANSFORMER: 1-f output; 455 kc.	CUP: capacitor-resistor; contains Cz. Ca, Cza, Ra, Ra; plastic.	CUP: capacitor-resistor; contains Ca. Caa. Ra; plastic.	CUP: capacitor-resistor; contains C14, C17, C14, C11, R12, R12, R13; pastic.	CUP: capacitor-resistor; contains Cas., Cas., Car., Ro., Rite, Rai., Raz; plastic.	ARM: switch lever (long); steel; (for late models SCR-536-CZE).
3RC20AE334K	3RC10AE223K	3RC10AR224K	3RC10AE684K	3RC20BE106K	3RC10AE335M	3RC10AE392K	3RC10AE682K	3RC20BEA75K	229641.8	229641.9	2C5351A/C4	2C5351A/C5	2CS351A/C3	2C5351A/C2	328318/1.5
R16	Rit	Ris	Ris	Rze	Ras	R24	R25	Rze	Tı	T2	2N1	2N2	282	ž,	

36-B, SCR-536-C, and SCR-536-D. (Cont.)

	Only maintenance parts listed can be requisitioned.								
Ref.	Signal Corps stock No.	Name of part and description	Ouan. per unit	Run- ning spares	Run- ning Orga spares stock	28 ech	44	5th ech	Depot
	328318/1.4	ARM: switch lever (hort); steel; (for late models SCR-536- CZE).	-						
	2C5351A/A6	BRACKET: tube retainer; (aluminum with rubber grommet).	00						
	221612.3	CAP ASSEMBLY: antenna; (with beaded 43s' chain).	-						
	28475/1	CAP: phone and microphone; molded baledite (for SCR-536- CZE).	60				٠		
	6G191.1	CEMENT: household; Duco.	-			•	•		
	2CE351C/C8	CHASSIS: for radio receiver and transmitter BC-611-C; com- pletely wired; fless tube shelds, tube retainers, washers, tubes, crystals, and plug-in colls).	-			•	•	•	•
	2SS36A/A3/7	CONTACT ASSEMBLY: battery; (part of cover disassembly).	-						
	223401.1	COVER: r-f choke; bakelite.	-						
	2SS36A/A3	COVER ASSEMBLY: bottom: (meduding battery contract as sembly, battery warning card, and seal).	-						
	2C5351C/C7	COVER: switch mechanism; modded neoprene; (for SCR-536- CZE).	-				٠		•
	2CS351C/A2	COVER ASSEMBLY: top: (includes insulator, antenna mois- ture and contact relate abott and arctical and subbas souline	-						

•		•	•	•	•	•		•	•			•	•	•	
1	1	1	-			-	-	-	-	-	1	-	1	1	
FERRULE: antenna guide.	FILLER AND CLIPS ASSEMBLY: fiber: (battery BA:38 spacer).	FRAME: cover clamping; aluminum.	GREASE: lubri plate.	GROOVE PIN: steel.	GUIDE: antenna; bakelite.	HANGER: strap; aluminum rod.	HINGE: fulcrum; steel (for SCR-536-CZE).	HINGE ASSEMBLY: fulcrum.	HOUSING: (less all parts).	HOUSING ASSEMBLY: (includes bottom cover, retainer, name plate, data plate, battery compartment filler, and press-to-talk mechanism).	INSULATOR ASSEMBLY: antenna; polystyrene; vinylite mossture seal; (for SCR-536-CZE).	JELLY: petroleum.	LINK: sliding hinge; steel; (for SCR-536 CZE).	LINK ASSEMBLY: sliding hinge.	COURS At oppose
2A1101	2C5351A/J2/7	2CESSIC/FI	66673	2SS35A/A3/2	2A292-2/4	2Z4976	3Z8138/H2	3Z8138/H3	2S5351A/J2.1	2C8351C/A1	3G1839-31	6G2205.2	328138/1.6	328138/L7	dores .

*Indicates stock available.

PIN: hinge; threaded; (press-to-tal

	Only maintenanc	Only maintenance parts listed can be requisitioned.							
Ref.	Signal Corps stock No.	Name of part and description	Ouan. per unit	Ouan. Run- per ning Orgn unit spares stock	Orga	8 db	45 th	Sch ech	Depc
	3Z8318/P2	PIN: hinge; (press-to-talk switch).	1						
	2C5351A/J1	PLUG: jumper; (molded bakelite over wire jumper).	-			•	•		•
	2SE36A/A2/2	ROD: long: (bottom) housing hinge rod and strap support; threaded.	-		•	•	•	•	•
	2SE36A/A2/3	ROD; short; (top) housing hinge rod and strap support; threaded.	1			•	•		•
	6L6540-4.9BS	SCREW: machine; switch mounting.	9			٠	•		•
	6L6632.6.9DS	SCREW: machine; antenna guide.	1				•		•
	61,7947	SCREW: self-tapping antenna cap.	1				•	••	
	61.6832-7.945	SCREW: top cover.	-				•	•	•
	2S536A/A3/5	SEAL: rubber ring; top and bottom cover.	61				•	•	•
	2S536A/S1	SLEEVE: rubber (part of stop cushion).	-						•
	1/88-680622	SLIDE: steel; carrying strap.	1			•	•	•	•
	228674.2	SOCKET: (crystal; 2-crystal receptade; mica-filled bakelite).	-				٠	•	•
	9-6998772	SOCKET: tube; 7-prong miniature.	07				٠		
	2CS351A/J2/5	SPADE BOLT AND COVER NUT ASSEMBLY: (holds bot-	1						•

SPRING: coll: returner.
SPRING: locking: (for late models SCB-53847ZE)
STRAP ASSEMBLY: carrying; (includes slide, strap hanger, and rods).
SUPPORT: wiper and socket.
SWITCH: press-to-talk; complete.
TUBE: JAN-IR5 (VT-171).
TUBE: JAN-1SS (VT-172).
TUBE: JAN-174 (VT-173).
TUBE: JAN-384 (VT-174).
WASHED, midden tolks established

•	•		•	•	•